

**UNIVERSITY OF CALIFORNIA, RIVERSIDE**  
**Department of Computer Science and Engineering**  
**Department of Electrical Engineering**  
**CS/EE120A – Logic Design**  
**Homework 2**  
**Given May 7, Due May 14, 2001**

16
----

1. Use the tabulation method to simplify the function  $f(w,x,y,z) = \Sigma(0,2,5,7,13,15)$ . List all the PI's, EPI's, cover lists, and solutions. (4)
2. Use only 2-to-1 multiplexers to implement the function  $f(w,x,y,z) = \Sigma(0,2,5,7,13,15)$ . Do not simplify it. (4)
3. Use VHDL to design an 8-bit wide tri-state buffer. (4)
4. Use basic gates to design a 3-to-8 decoder. (4)