

CS/EE 120A

Homework #3 Given 3/6/01. Due 3/13/01



1. Use only 4 CMOS transistors to draw the circuit for the XOR gate.

Not graded

(4)

Answer

XOR

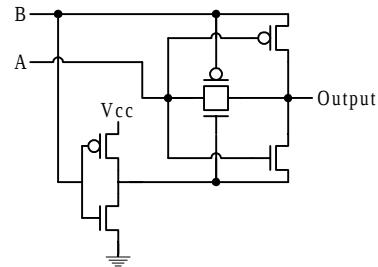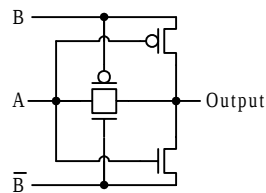

(I was wrong in telling some students that if they use both the non-inverted and inverted signals, they have to add two more inverters. So if you use only inputs A and B, then your circuit will have 6 transistors like the circuit on the right. Otherwise, it is like the circuit on the left.)

2. Write the function that eliminates the static hazard(s) in the function $F = w'z + xyz' + wx'y$

(4)

Answer

yz \ wx	00	01	11	10
00	0	1	1	2
01	4	1	1	6
11	12	13	15	14
10	8	9	11	10


Original function

yz \ wx	00	01	11	10
00	0	1	1	2
01	4	1	1	6
11	12	13	15	14
10	8	9	11	10

After adding the overlaps

$$F = w'z + xyz' + wx'y + w'xy + wyz' + x'yz$$

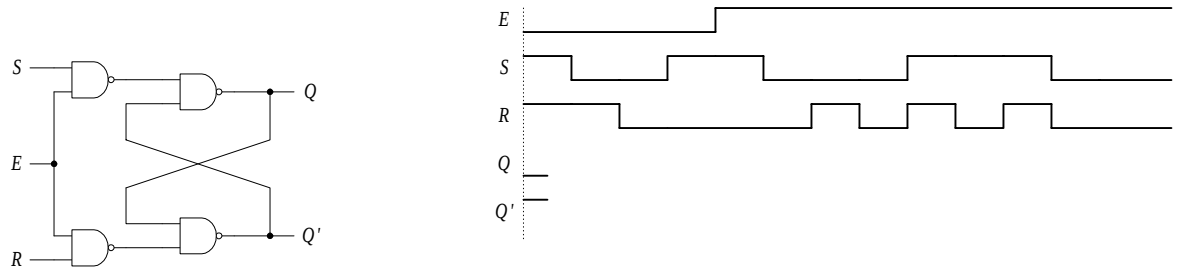3. Given the following circuit and trace for the inputs of the circuit, draw the trace for the outputs Q and Q' . (4)



Answer

