

UNIVERSITY OF CALIFORNIA, RIVERSIDE
Department of Computer Science and Engineering
Department of Electrical Engineering
CS/EE120A – Logic Design
Midterm 2
February 22, 2001

30

Name: Solution Key Student ID#: _____

Please print legibly

Lab Section: 21 (MW 3-6): _____ 22 (TR 2-5): _____ 23 (MF 8-11): _____

(Numbers in parenthesis denote total possible points for question.)

1. Use the tabulation method to find the PI list and the EPI list for the function (5)

$$f = w'x'y'z' + xy'z + w'xz + wxy.$$

Answer

The 1-minterms are: $m_0, m_5, m_7, m_{13}, m_{14}, m_{15}$.

List of 0-subcubes:

Group ID	Subcube Minterms	Subcube Value				Subcube Covered
		w	x	y	z	
G_0	m_0	0	0	0	0	
G_2	m_5	0	1	0	1	yes
G_3	m_7	0	1	1	1	yes
	m_{13}	1	1	0	1	yes
	m_{14}	1	1	1	0	yes
G_4	m_{15}	1	1	1	1	yes

List of 1-subcubes:

Group ID	Subcube Minterms	Subcube Value				Subcube Covered
		w	x	y	z	
G_2	$m_{5,7}$	0	1	-	1	yes
	$m_{5,13}$	-	1	0	1	yes
G_3	$m_{7,15}$	-	1	1	1	yes
	$m_{13,15}$	1	1	-	1	yes
	$m_{14,15}$	1	1	1	-	

List of 2-subcubes:

Group ID	Subcube Minterms	Subcube Value				Subcube Covered
		w	x	y	z	
G_2	$m_{5,7,13,15}$	-	1	-	1	

The PI list is: $xz, wxy, w'x'y'z'$

Prime Implicant Name	Prime Implicant Expression	Implicant Minterms	Function Minterms					
			0	5	7	13	14	15
P_1	xz	(14,15)					$\otimes$	$\times$
P_2	wxy	(5,7,13,15)		$\otimes$	$\otimes$	$\otimes$		$\times$
P_3	$w'x'y'z'$	(0)	$\otimes$					
EPI covered minterms:			0	5	7	13	14	15
Not covered minterms:								

The EPI list is: xz , wxy , $w'x'y'z'$

☞ 2 points if PI and EPI lists are obtained using K-maps.

2. Derive the minimized equations for the full subtractor circuit. Draw the full subtractor circuit using only 2-input basic gates (AND, OR, NOT, XOR) from the minimized equations. Your circuit should use as few gates as possible. (5)

Answer

The full subtractor truth table is


b_{in}	x	y	b_{out}	d
0	0	0	0	0
0	0	1	1	1
0	1	0	0	1
0	1	1	0	0
1	0	0	1	1
1	0	1	1	0
1	1	0	0	0
1	1	1	1	1

Thus, the minimized equations are:

$$b_{out} = b_{in}x' + b_{in}y + x'y$$

$$d = b_{in} \oplus x \oplus y$$

The circuit is

 

3. Derive the equation for the carry lookahead signal c_3 in terms of the two operand inputs x and y , and c_0 . (5)

Answer

$$c_{i+1} = g_i + p_i c_i$$

$$c_1 = g_0 + p_0 c_0$$

$$\begin{aligned} c_2 &= g_1 + p_1 c_1 \\ &= g_1 + p_1(g_0 + p_0 c_0) \\ &= g_1 + p_1 g_0 + p_1 p_0 c_0 \end{aligned}$$

$$\begin{aligned} c_3 &= g_2 + p_2 c_2 \\ &= g_2 + p_2(g_1 + p_1 g_0 + p_1 p_0 c_0) \\ &= g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0 \end{aligned}$$

Substituting $g_i = x_i y_i$ and $p_i = x_i + y_i$ into c_3 , we get

$$c_3 = x_2 y_2 + (x_2 + y_2)x_1 y_1 + (x_2 + y_2)(x_1 + y_1)x_0 y_0 + (x_2 + y_2)(x_1 + y_1)(x_0 + y_0)c_0$$


4. Design a 4-bit ALU that satisfies the following functional table:

M	S_1	S_0	Function
0	0	0	$A \text{ AND } B$
0	0	1	$A \text{ XOR } B$
0	1	0	All 0's, i.e. clear the output
0	1	1	Pass through operand A
1	0	0	Subtract $A - B$
1	0	1	Decrement A
1	1	0	not used
1	1	1	not used

The AE and LE circuits must be simplified. You need to draw the complete ALU circuit. (15)

Answer:

 The overall general 4-bit ALU circuit is as follows:




The truth table for the LE, AE, and CE according to the given functions is shown next:

M	S_1	S_0	Function	LE x_i	AE y_i	CE c_0
0	0	0	$A \text{ AND } B$	$a_i b_i$	0	0
0	0	1	$A \text{ XOR } B$	$a_i \oplus b_i$	0	0
0	1	0	All 0's, i.e. clear the output	0	0	0
0	1	1	Pass through operand A	a_i	0	0
1	0	0	Subtract $A - B$	a_i	b_i'	1
1	0	1	Decrement A	a_i	all 1's	0
1	1	0	not used	$\times$	$\times$	$\times$
1	1	1	not used	$\times$	$\times$	$\times$

The K-Map, equation and circuit for the LE is as follows:


x_i $a_i b_i$ $S_1 S_0$		$M = 0$				$M = 1$			
		00	01	11	10	00	01	11	10
00		0	1	3	2	16	17	19	18
01		4	5	7	6	20	21	23	22
11		12	13	15	14	28	29	31	30
10		8	9	11	10	24	25	27	26

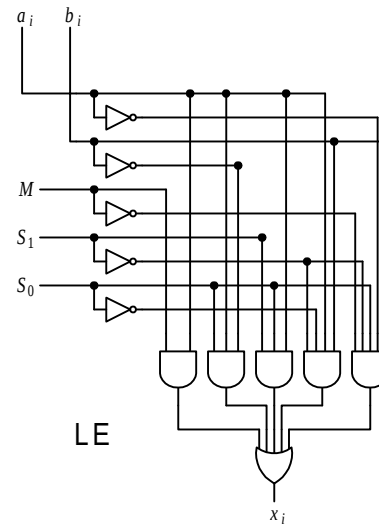

$$x_i = Ma_i + S_0 a_i b_i' + S_1 S_0 a_i + S_1' S_0' a_i b_i + M' S_1' S_0 a_i' b_i$$

The K-Map, equation and circuit for the AE is as follows:


y_i $S_0 b_i$ $M S_1$		00	01	11	10
		00	01	11	10
00		0	1	3	2
01		4	5	7	6
11		12	13	15	14
10		8	9	11	10

 

$$y_i = MS_0 + Mb_i'$$

The K-Map, equation and circuit for the CE is as follows:

c_0 $S_1 S_0$ M		00	01	11	10
		00	01	11	10
0		0	1	3	2
1		4	5	7	6

 

$$c_0 = MS_0'$$