

Lab 8

Datapath Design

Objectives

- To get familiar with the Xilinx VHDL Editor Tool.
- To design and implement an ALU circuit using VHDL at the Behavioral level.
- Simulate and test combinational circuits.
- To download your circuit onto the prototype board and test it.


Laboratory Instructions

- Use the Xilinx VHDL editor to create the VHDL source file(s) for your design before coming to the lab.
- Create a directory with your name on drive C of your lab PC. Use this directory to create your project, store your results, bitstreams, etc. during the lab session.
- You can bring a complete project (i.e. *project.pdf* file and *project* directory) on a floppy disk and then use the **Copy Project** command from the Project Manager menu to copy it into the directory you created above.
- Alternatively, you can create a new project in your directory on the C drive and then copy your files to that new project directory. Remember to *Add* your VHDL file to the project.
- Perform functional simulation of your design and have it checked by your TA.
- If the circuit works as expected, implement it using the prototyping board assigned to you.
- Use keyboard and LEDs available to apply input stimuli and observe the outputs. Disconnect the XSPORT (parallel port) when you apply input stimulus from the workbench.
- Test and demonstrate your circuit to your TA.

Design Problems

Using the Xilinx VHDL Editor, design, test and demonstrate the following circuits. Your circuits should be as small as possible.

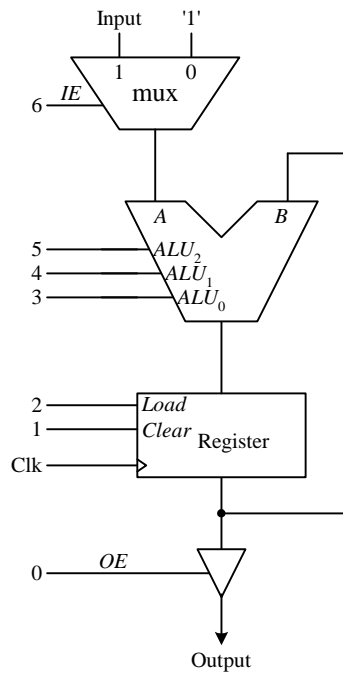1. Implement the following 4-bit datapath at the Structural level. All the components in the datapath are those that you have designed in the previous labs.



Test the circuit with the counting program that outputs the numbers from 0 to 9 as presented in class.