

VHDL is an abbreviation for Very High Speed Integrated Circuit Hardware Description Language, and is used for modeling digital systems. VHDL coding includes *behavior modeling*, *structure modeling* and *dataflow modeling*. After studying the following simple examples, you will quickly become familiar with its syntax and reserved words (in bold). Please note that these codes are only for your reference, NOT the exact solution for EE/CS120A's Hwk/Lab/Project. However, if you spend some time to understand all of them, it could be very helpful, even for the future class EE/CS120B. Have fun!

(1) D Flip-Flop with Asynchronous Reset

```
library IEEE;
use IEEE.std_logic_1164.all;

entity dff_async_rst is
    port( data, clk, reset: in    std_logic;
          q:           out   std_logic);
end dff_async_rst;

architecture behav of dff_async_rst is
begin
process(clk,reset)
begin
    if (reset='0') then
        q<='0';
    elsif (clk'event and clk='1') then
        q<=data;
    end if;
end process;
end behav;
```

(2) 4:1 Multiplexor

```
library IEEE;
use IEEE.std_logic_1164.all;

entity mux is
    port( c,d,e,f:    in    std_logic;
          s:           in    std_logic_vector(1 downto 0);
          muxout:       out   std_logic);
end mux;

architecture my_mux of mux is
begin
mux1: process(s,c,d,e,f)
begin
    case s is
        when "00"=> muxout <= c;
        when "01"=> muxout <= d;
        when "10"=> muxout <= e;
        when others => muxout <= f;
    end case;
end process mux1;
end my_mux;
```

(3) Shift Register

```
library IEEE;
use IEEE.std_logic_1164.all;

entity shift is
    port( d_in,clk,resetn:  in      std_logic;
          d_out:           out      std_logic );
end shift;

architecture shift_reg of shift is
begin
process(clk,d_in,d_out)
    variable REG: std_logic_vector(2 downto 0):=('0','0','0');
begin
    if resetn='0' then REG (2 downto 0):=('0','0','0');
    elsif clk 'event and clk='1' then
        REG:= d_in & REG(2 downto 1);
    end if;
    d_out<=REG(0);
end process;
end shift_reg;
```

(4) 4-bit Up Counter with Enable and Asynchronous Reset

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
use IEEE.std_logic_arith.all;

entity counter4 is
    port( clk,en,rst:      in      std_logic;
          count:           out      std_logic_vector(7 downto 0));
end counter4;

architecture behav of counter4 is
signal cnt: std_logic_vector (3 downto 0);
begin
process(clk,en,cnt,rst)
begin
    if (rst='0') then
        cnt <= (others =>'0');
    elsif (clk'event and clk='1') then
        if (en='1') then
            cnt <= cnt+'1';
        end if;
    end if;
end process;
count <= cnt;
end behav;
```

(5) 2-4 Decoder

```
library IEEE;
use IEEE.std_logic_1164.all;

entity decode is
    port( Ain:  in      std_logic_vector(1 downto 0);
          En:   in      std_logic;
          Yout: out     std_logic(3 downto 0));
end decode;

architecture decode_arch of decode is
begin
process(Ain)
begin
    if (En='0') then
        Yout <= (others=>'0');
    else
        case Ain is
            when "00"=> Yout<="0001";
            when "01"=> Yout<="0010";
            when "10"=> Yout<="0100";
            when "11"=> Yout<="1000";
        end case;
    end if;
end process;
end decode_arch;
```

(6) 8-bit Comparator/Comparator Cell

```
library IEEE;
use IEEE.std_logic_1164.all;

entity cmp_cell is
port( a,b:  in      std_logic;
      Cin:  in      std_logic_vector(1 downto 0);
      Cout: out     std_logic_vector(1 downto 0));
end decode;

architecture cmp_cell of cmp_cell is
begin
process(Cin,a,b)
begin
    if Cin="10" then Cout<="10";
    elsif Cin="01" then Cout<="01";
    elsif Cin="00" and a=b then Cout<="00";
    elsif Cin="00" and a>b then Cout<="01";
    elsif Cin="00" and a<b then Cout<="10";
    end if;
end process;
end cmp_cell;

library IEEE;
use IEEE.std_logic_1164.all;
```

```

entity comparator_8 is
port(
    A,B:      in      std_logic_vector(7 downto 0);
    CMPIN:    in      std_logic_vector(1 downto 0);
    CMPOUT:   out     std_logic_vector(1 downto 0));
end comparator_8;

architecture cmp_8 of comparator_8 is
component cmp_cell
port(
    a,b:      in      std_logic;
    Cin:     in      std_logic_vector(1 downto 0);
    Cout:    out     std_logic_vector(1 downto 0));
end component;
signal OUT0,OUT1,OUT2,OUT3,OUT4,OUT5,OUT6:std_logic_vector(1 downto 0);
begin
    cell0:cmp_cell port map(A(0),B(0),CMPIN,OUT0);
    cell1:cmp_cell port map(A(1),B(1),OUT0,OUT1);
    cell2:cmp_cell port map(A(2),B(2),OUT1,OUT2);
    cell3:cmp_cell port map(A(3),B(3),OUT2,OUT3);
    cell4:cmp_cell port map(A(4),B(4),OUT3,OUT4);
    cell5:cmp_cell port map(A(5),B(5),OUT4,OUT5);
    cell6:cmp_cell port map(A(6),B(6),OUT5,OUT6);
    cell7:cmp_cell port map(A(7),B(7),OUT6,CMPOUT);
end cmp_8;

```

(7) Finite State Machine

```

library IEEE;
use IEEE.std_logic_1164.all;

entity sequence is
port( clk,resetn,data_in:      in      std_logic;
      data_out:                 out     std_logic);
end sequence;

architecture state_machine of SEQUENCE is
    type StateType is (ST0,ST1,ST2,ST3,ST4,ST5,ST6,ST7);
    signal Current_State:StateType;
begin
state_comb: process(clk,resetn, Current_State)
    variable REG: std_logic_vector(2 downto 0);
begin
    if clk 'event and clk='1' and resetn='1' then
        case Current_State is
            when ST0 =>
                if data_in='0' then Current_State<=ST0;
                else Current_State<=ST1;
                end if;
            when ST1 =>
                if data_in='0' then Current_State<=ST2;
                else Current_State<=ST3;
                end if;
            when ST2 =>
                if data_in='0' then Current_State<=ST4;
                else Current_State<=ST5;
                end if;
        end case;
    end if;
end process;

```

```
        end if;
when ST3 =>
    if data_in='0' then Current_State<=ST6;
    else Current_State<=ST7;
    end if;
when ST4 =>
    if data_in='0' then Current_State<=ST0;
    else Current_State<=ST1;
    end if;
when ST5 =>
    if data_in='0' then Current_State<=ST0;
    else Current_State<=ST1;
    end if;
when ST6 =>
    if data_in='0' then Current_State<=ST4;
    else Current_State<=ST5;
    end if;
when ST7 =>
    if data_in='0' then Current_State<=ST6;
    else Current_State<=ST7;
    end if;
end case;
REG:=data_in&REG(2 downto 1);
elsif resetn='0' then
    Current_State<=ST0;
    REG(2 downto 0):=(‘0’,‘0’,‘0’);
end if;
data_out<=REG(0);
end process state_comb;
end architecture state_machine;
```