


CS120B – Homework #2

Given November 2, 2001. Due November 8, 2001

- Construct a FSM that realizes the following algorithm based on the datapath below.

Input two numbers.

Output the product of the two numbers.

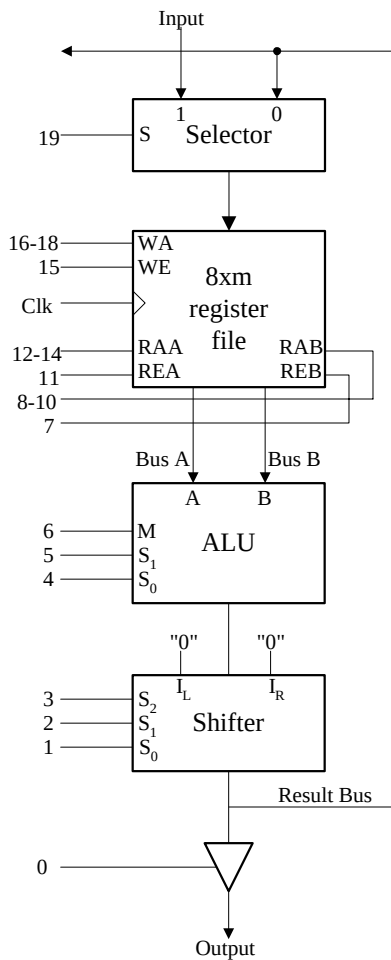

M	S ₁	S ₀	ALU operations
0	0	0	Complement A
0	0	1	AND
0	1	0	XOR
0	1	1	OR
1	0	0	Decrement A
1	0	1	Add
1	1	0	Subtract
1	1	1	Increment A

ALU operations

S ₂	S ₁	S ₀	Shift operations
0	0	0	Pass
0	0	1	Pass
0	1	0	Not used
0	1	1	Not used
1	0	0	Shift left
1	0	1	Rotate left
1	1	0	Shift right
1	1	1	Rotate right

Shift operations

Answer


Algorithm

```
1  sum = 0
2  input x
3  input y
   while y <> 0
4    sum = sum + x
5    y = y - 1
6  output sum
```

Control words

	19	18-15	14-11	10-7	6-4	3-1	0	
Control words	IE	Write	Read A	Read B	ALU operation	Shifter operation	OE	Comment
1	0	010 1	000 1	000 1	010	000	0	$x \text{ xor } x = 0$
2	1	001 1	xxx 0	xxx 0	xxx	xxx	0	input x
3	1	000 1	xxx 0	xxx 0	xxx	xxx	0	input y
4	0	010 1	010 1	001 1	101	000	0	$\text{sum} += x$
5	0	000 1	000 1	xxx x	100	000	0	decrement A
6	0	xxx 0	010 1	010 1	001	000	1	sum and sum <=> pass

State diagram

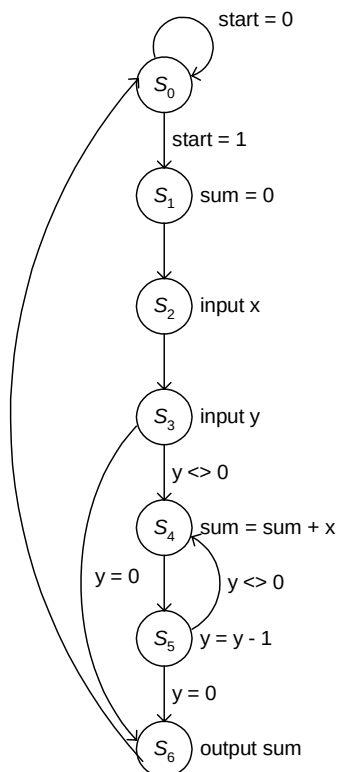

Next-state table:

Current State		Next State			
Sym bol	Q_2 Q_1 Q_0	Start, ($y <> 0$)			
		00	01	10	11
s_0	0 0 0	0 0 0	0 0 0	0 0 1	0 0 1
s_1	0 0 1	0 1 0	0 1 0	0 1 0	0 1 0
s_2	0 1 0	0 1 1	0 1 1	0 1 1	0 1 1
s_3	0 1 1	1 1 0	1 0 0	1 1 0	1 0 0
s_4	1 0 0	1 0 1	1 0 1	1 0 1	1 0 1
s_5	1 0 1	1 1 0	1 0 0	1 1 0	1 0 0
s_6	1 1 0	0 0 0	0 0 0	0 0 0	0 0 0

Next-state equations:

Q_{1next} Q_1Q_0	Start, ($y \neq 0$)		$Q_2 = 0$				$Q_2 = 1$			
	00	01	11	10	00	01	11	10		
00	0	0	1	1	1	1	1	1		
01	0	0	0	0	0	0	0	0		
11	0	0	0	0	×	×	×	×		
10	1	1	1	1	0	0	0	0		

$$Q_{0next} = Q_2'Q_1Q_0' + Q_2Q_1'Q_0' + Q_1'Q_0'Start$$

Q_{1next} Q_1Q_0	Start, ($y \neq 0$)		$Q_2 = 0$				$Q_2 = 1$			
	00	01	11	10	00	01	11	10		
00	0	0	0	0	0	0	0	0		
01	1	1	1	1	1	0	0	1		
11	1	0	0	1	×	×	×	×		
10	1	1	1	1	0	0	0	0		

$$Q_{1next} = Q_2'Q_1Q_0' + Q_2'Q_1'Q_0 + Q_0(y \neq 0)'$$

Q_{2next} Q_1Q_0	Start, ($y \neq 0$)		$Q_2 = 0$				$Q_2 = 1$			
	00	01	11	10	00	01	11	10		
00	0	0	0	0	1	1	1	1		
01	0	0	0	0	1	1	1	1		
11	1	1	1	1	×	×	×	×		
10	0	0	0	0	0	0	0	0		

$$Q_{2next} = Q_1Q_0 + Q_2Q_0'$$

Output equations:

$$IE = Q_2'Q_1Q_0' + Q_2'Q_1Q_0$$

$$WA_2 = 0$$

$$WA_1 = Q_2'Q_1'Q_0 + Q_2Q_1'Q_0'$$

$$WA_0(Q_2, Q_1, Q_0) = \Sigma(2)$$

$$WE(Q_2, Q_1, Q_0) = \Sigma(1, 2, 3, 4, 5)$$

$$RAA_2 = 0$$

$$RAA_1 = Q_2 Q_1' Q_0'$$

$$RAA_0 = 0$$

$$RAE(Q_2, Q_1, Q_0) = \Sigma(1, 4, 5, 6)$$

etc...

FSM Schematic

