

UNIVERSITY OF CALIFORNIA, RIVERSIDE
Department of Computer Science and Engineering
Department of Electrical Engineering
CS/EE120B – Introduction to Embedded Systems

24

Final

Thursday June 14, 2001 8AM – 11AM

Name: **Solution Key** **Student ID#:** _____
Please print legibly

Lab Section: 21 (TR 6-10): _____ 22 (WF 6-10): _____ 23 (WF 2-6): _____

(Numbers in parenthesis denote total possible points for question.)

1. Discuss whether a flip-flop can be used as an input port for a general microprocessor system if the output of a flip-flop is connected directly to the system data bus. Give your reasons as to why it can or cannot be used. (4)

Answer

No. Since the flip-flop always outputs a value (0 or 1), the data bus is never released for other input devices to use. An input port requires a tri-state buffer where it can be disabled and outputs a “Z” value.


2. Draw the FSM using D flip-flops for the following next-state equations. The states are encoded using the straight sequential binary numbers. Using a 4-bit datapath, draw also the circuits to assert the required status signals used in the next-state equations. (4)

$$Q_{0next} = s_0Start + s_2 + s_6(n = 10)$$


$$Q_{1next} = s_2 + s_4(n \neq 10)$$

$$Q_{2next} = s_1 + s_2Start' + s_3(n = 3)$$

Answer

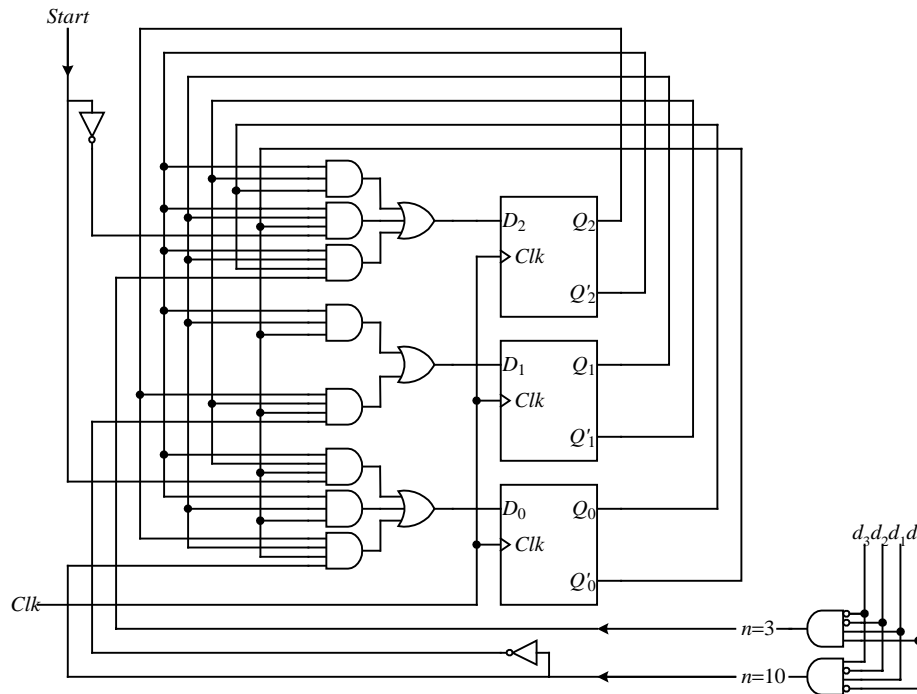

 3. The following questions refer to the following 3-to-8 decoder circuit. Assume that the CPU that this circuit is connected to has 16 address lines (A0 to A15). Specify all addresses in hex. (4)



- What is the lowest address (in hex) that will assert the output line Y_3 ?
- What is the highest address (in hex) that will assert the output line Y_3 ?
- What is the highest address (in hex) that will assert the output line Y_3 if A7 to A15 are all 0's?
- Will the address 0AB7 (in hex) assert the output line Y_3 ? If no, then which output line will it assert?

Answer

011 for the three address lines A6, A5, and A3 will assert Y_3 .

The lowest address will be when the rest of the address lines are 0.

The highest address will be when the rest of the address lines are 1.

	A15	A14	A13	A12	A11	A10	A9	A8	A7	A6	A5	A4	A3	A2	A1	A0
a)	0	0	0	0	0	0	0	0	0	0	1	0	1	0	0	0
b)	1	1	1	1	1	1	1	1	1	0	1	1	1	1	1	1
c)	0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1
d)	0	0	0	0	1	0	1	0	1	0	1	1	0	1	1	1

- 0028 hex
- FFBF hex
- 003F hex
- No, Y_2 is asserted because the three address bits A6,A5,A3 are 010.

4. Synthesize (construct) a JK flip-flop using a T flip-flop. i.e. construct a circuit using a T flip-flop and two inputs (J and K) to the circuit that has the same behavior (truth table) as the JK flip-flop. (4)

Answer

The JK truth table is

J	K	Q	Q_{next}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

Re-write the JK truth table as a next-state table

	Q_{next}			
Q	JK = 00	JK = 01	JK = 11	JK = 10
0	0	0	1	1
1	1	0	0	1

The T excitation table is


Q	Q_{next}	T
0	0	0
0	1	1
1	0	1
1	1	0

The implementation table is obtained by substituting the values from the T excitation table into the JK next-state table.

	T			
Q	JK = 00	JK = 01	JK = 11	JK = 10
0	0	0	1	1
1	0	1	1	0

From the T flip-flop implementation table, we get the following equation and circuit.

$$T = QK + Q'J$$

 


5. Which of the three datapaths shown below cannot be used to implement the following algorithm? Check all the datapaths that applies. For each datapath that you check, circle the extra or missing parts in the datapath that are wrong and give a brief reason as to why the datapath won't work. In the datapath schematics, all data lines are 8 bits and all signal lines are 1 bit except where noted. (4)

```


sum = 0
input n
for i = 1 to n
    if (i mod 2) == 0
        sum = sum + 1
output sum

```


a)

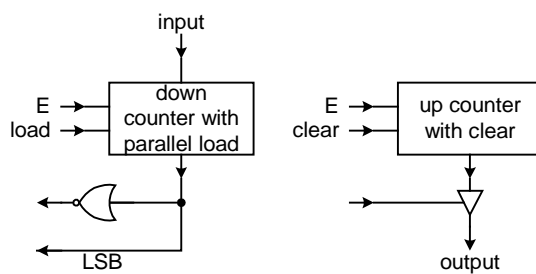

b)

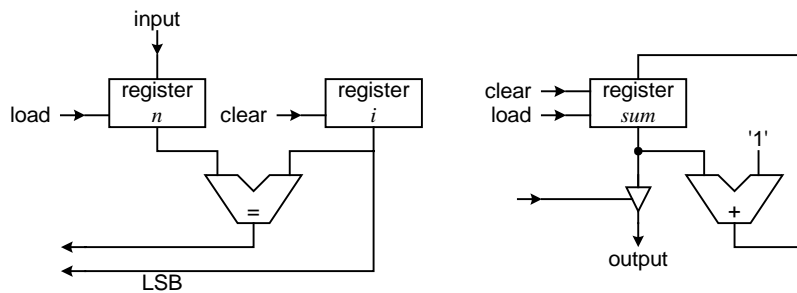


c)

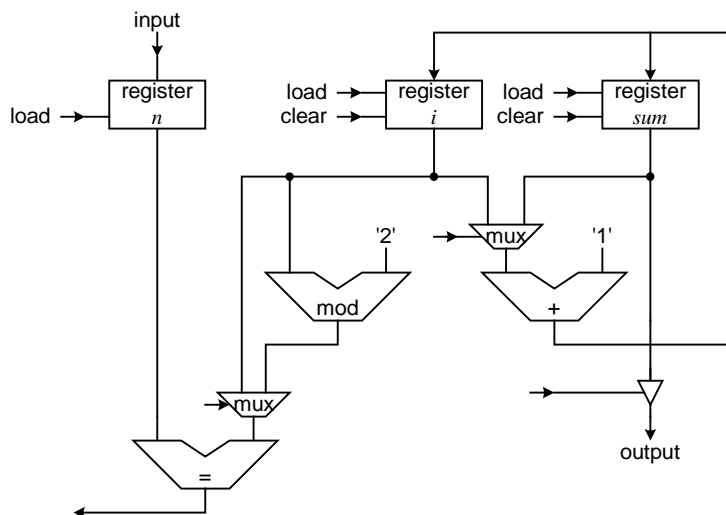

6. Derive the state diagram for the following sequential circuit

(4)

 

Answer

Excitation equations:

$$D_1 = Q_1 Q_0' Q_0 + Start' Q_1' Q_0' (n=10)'$$

$$= Start' Q_1' Q_0' (n=10)'$$

$$J_0 = (n=10)' Q_1' Q_0' Start + Q_0 Q_1 Q_0' + (n=0) Q_1 Q_0' (n=10)$$

$$= (n=10)' Q_1' Q_0' Start$$

$$K_0 = (n=0)$$

Characteristic equations:

$$Q_{1next} = D_1$$

$$Q_{0next} = K_0' Q_0 + J_0 Q_0'$$

We get the next-state equations by substituting the excitation equations into the characteristic equations:

$$Q_{1next} = D_1 = Start' Q_1' Q_0' (n=10)'$$

$$Q_{0next} = K_0' Q_0 + J_0 Q_0'$$

$$= (n=0)' Q_0 + (n=10)' Q_1' Q_0' Start Q_0'$$

$$= (n=0)' Q_0 + (n=10)' Q_1' Q_0' Start$$

Next-state table:

Current State $Q_1 Q_0$	Next State $Start, (n=0), (n=10)$							
	000	001	010	011	100	101	110	111
00	00	00	00	00	10	00	10	00
01	01	01	00	00	01	01	00	00
10	00	00	00	00	00	00	00	00
11	01	01	00	00	01	01	00	00

State diagram:

