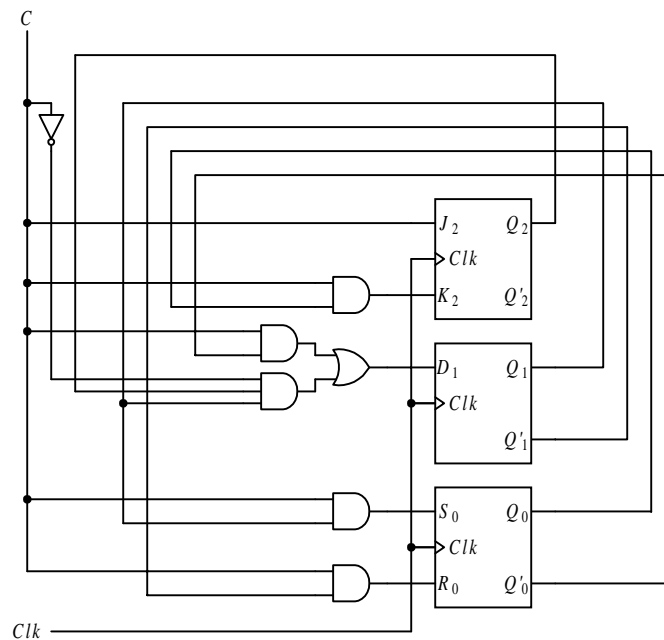


UNIVERSITY OF CALIFORNIA, RIVERSIDE
Department of Computer Science and Engineering
Department of Electrical Engineering
CS/EE120B – Introduction to Embedded Systems
Homework 1

15

Given April 9, 2001, Due April 18, 2001


1. Derive the next-state/output table and state diagram for the following circuit. (5)



Answer

Current State $Q_2Q_1Q_0$	Next State	
	$Q_{2next} \ Q_{1next} \ Q_{0next}$	
	$C = 0$	$C = 1$
001	001	100
100	100	110
110	110	111
111	111	001

3 points for
getting this.

 

2 points for
getting this

2. Synthesize a circuit that will count the following sequence using only one type of flip-flops:

1, 4, 6, 7, 1, 4, 6, 7,

The count is to be represented directly by the contents of the flip-flops. The counter is enabled by the input C . The count stops when $C = 0$. Determine which type of flip-flop (D, SR, JK, or T) gives the smallest circuit. You only need to draw the circuit using the flip-flops that gives the smallest circuit. Assume that the circuit size is proportional to the number of 2-input gates and inverters needed in the next-state function. (10)

Answer

The next-state table and D implementation table is:

Current State $Q_2Q_1Q_0$	Next State		
	Q_{2next}	Q_{1next}	Q_{0next}
	$C = 0$	$C = 1$	
001	001	100	
100	100	110	
110	110	111	
111	111	001	

The equations are:

$$D_2 = CQ_1' + C'Q_2 + Q_1Q_0'$$

$$D_1 = C'Q_1 + CQ_2Q_0'$$

$$D_0 = C'Q_0 + CQ_2Q_1$$

Requires 13 2-input gates + 1 inverter

The SR implementation table is:

Current State $Q_2Q_1Q_0$	Implementation $S_2R_2 S_1R_1 S_0R_0$	
	$C = 0$	$C = 1$
001	0×0××0	100×01
100	×00×0×	×0100×
110	×0×00×	×0×010
111	×0×0×0	0101×0

The equations are:

$$S_2 = CQ_2'$$

$$R_2 = CQ_2Q_0$$

$$S_1 = CQ_2Q_1'$$

$$R_1 = CQ_0$$

$$S_0 = CQ_1$$

$$R_0 = CQ_1$$

Requires 8 2-input gates + 0 inverters

The JK implementation table is:

Current State $Q_2Q_1Q_0$	Implementation $J_2K_2 J_1K_1 J_0K_0$	
	$C = 0$	$C = 1$
001	0×0××0	1×0××1
100	×00×0×	×01×0×
110	×0×00×	×0×01×
111	×0×0×0	×1×1×0

+ 5 points for
this

The equations are:

$$J_2 = C$$

$$K_2 = CQ_0$$

$$J_1 = CQ_2$$

$$K_1 = CQ_0$$

$$J_0 = CQ_1$$

$$K_0 = CQ_2'$$

+ 2 points for
this

Requires 4 2-input gates + 0 inverters

The T implementation table is:

Current State $Q_2Q_1Q_0$	Implementation $T_2T_1T_0$	
	$C = 0$	$C = 1$
001	000	101
100	000	010
110	000	001
111	000	110

The equations are:


$$T_2 = CQ_0$$

$$T_1 = CQ_2Q_1' + CQ_2Q_0$$

$$T_0 = CQ_2' + CQ_1Q_0'$$

Requires 10 2-input gates + 0 inverters

 Using the JK flip-flop produces the smallest circuit size as shown below.



+ 3 points for
this. i.e.

only need this
circuit to get
full points.