

**UNIVERSITY OF CALIFORNIA, RIVERSIDE**  
**Department of Computer Science and Engineering**  
**Department of Electrical Engineering**  
**CS/EE120B – Introduction to Embedded Systems**  
**Final**  
**March 20, 2001**

**25**

Name: Solution Key Student ID#: \_\_\_\_\_  
*Please print legibly*

Lab Section: 21 (WF 6-10): \_\_\_\_\_ 22 (MW 2-6): \_\_\_\_\_ 23 (TR 6-10): \_\_\_\_\_

(Numbers in parenthesis denote total possible points for question.)

1. Design a T flip-flop using a SR flip-flop and basic gates. (5)

**Answer**

The next-state table for the T flip-flop is

	$Q_{next}$	
$Q$	T = 0	T = 1
0	0	1
1	1	0

Converting the next-state table to the implementation table for the SR flip-flop, we get

	SR	
$Q$	T = 0	T = 1
0	0 ×	1 0
1	× 0	0 1

1 point for correct implementation table

**Solution 1:**

$$S = TQ'$$



$$R = TQ$$

2 points for correct equations

**Solution 2:**

$$S = T \oplus Q$$

$$R = (T \oplus Q)'$$

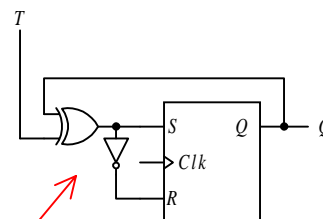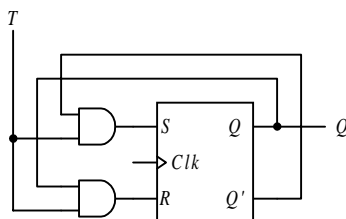

2 points for correct circuit

2. Synthesize the FSM circuit using T flip-flops for the following next-state / output table. (5)

Current State $Q_2Q_1Q_0$	Next State $Q_{2next} Q_{1next} Q_{0next}$		Output $Y$
	$C = 0$	$C = 1$	
000	000	001	0
001	001	010	0
010	010	011	0
011	011	100	0
100	100	101	0
101	101	000	1

**Answer**

The implementation table is as follows:

Current State $Q_2 Q_1 Q_0$	Implementation $T_2 T_1 T_0$	
	$C = 0$	$C = 1$
000	000	001
001	000	011
010	000	001
011	000	111
100	000	001
101	000	101

1 point for correct implementation table

The next-state / output equations are as follows:

$$T_2 = CQ_2'Q_1Q_0 + CQ_2Q_1'Q_0$$

$$= CQ_0(Q_2 \oplus Q_1)$$

$$T_1 = CQ_2'Q_1'Q_0 + CQ_2'Q_1Q_0$$


$$= CQ_2'Q_0$$

$$T_0 = C$$

$$Y = Q_2Q_1'Q_0$$

2 points for the four equations (0.5 points each).

The FSM circuit is as follows:

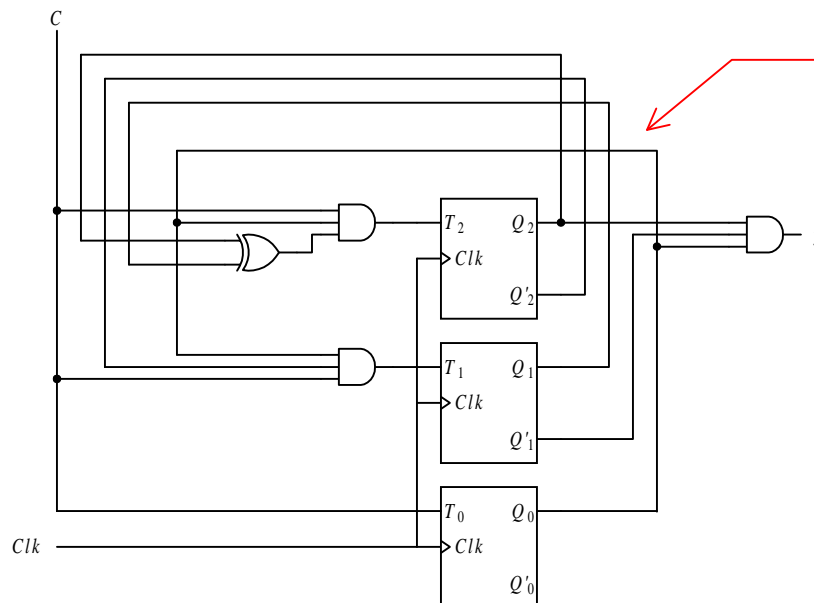

2 points for the correct circuit.

3. Design a customized datapath and a State-action table for the Mealy FSM that solves the following problem. Your datapath should use as few single functional units and registers as possible. Your FSM should have a *start* and a *done* signal. You should first write the high-level pseudo-code that solves the problem. (5)

Input (given) a 7-bit data. Output a '1' if there are odd number of 1 bits in the data, otherwise, output a '0'.

### Answer

```


even = 0;
input n;
while n ≠ 0{
    if (LSB(n) == 1)
        even = not even;
    n = n >> 1;
}
output even;
output done;

```

1 point for the pseudo-code

For the datapath, we need:

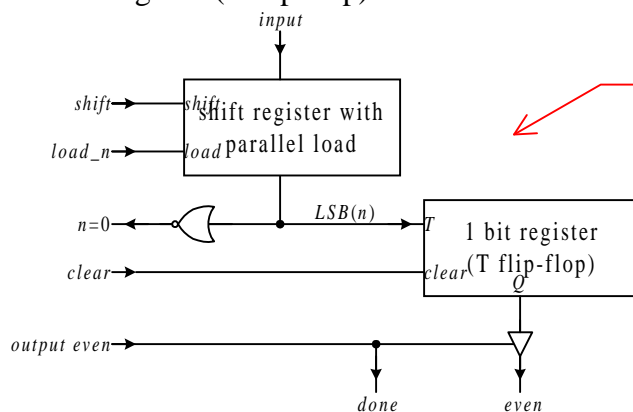- one shift register with parallel load for the variable  $n$ .
- a one bit register (T flip-flop) with load and clear for the variable  $even$ .



2 points for this datapath.

1 point only if the datapath uses more functional units like those shown below.


2 points for this state-action table.

The Mealy FSM is as follows:

Current State $Q_1 Q_0$ Name	Next State [Condition, State]	Control and Datapath Actions [Condition, Actions]
0 0 $s_0$	$[start = 0, s_0]$ $[start = 1, s_1]$	$even = 0$ $done = 0$ $output = Z$
0 1 $s_1$	$s_2$	$n = input$
1 0 $s_2$	$[n \neq 0, s_2]$ $[n = 0, s_3]$	$[LSB(n) = 1, even = not\ even]$ $[n \neq 0, n = n >> 1]$
1 1 $s_3$	$s_0$	$output = even$ $done = 1$

Other possible datapath:

Datapath 2:

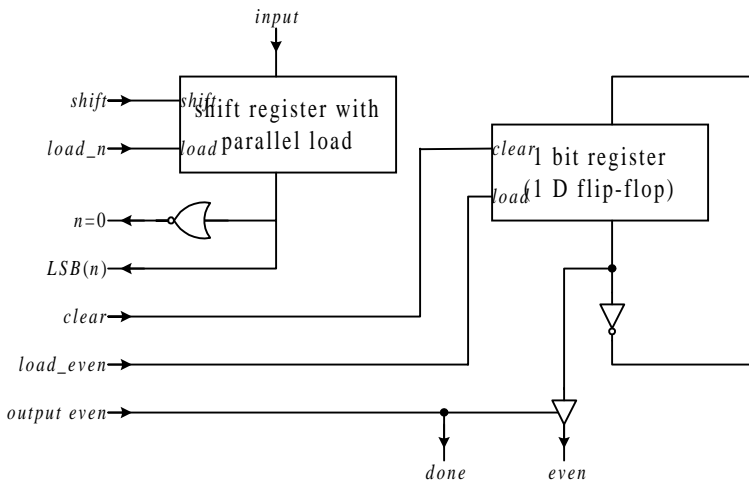


Datapath 3:

Algorithm: Using a counter to count the number of ones and a “divider” to divide by two to see if it is even or odd.

Functional units require: counter, divider, comparator

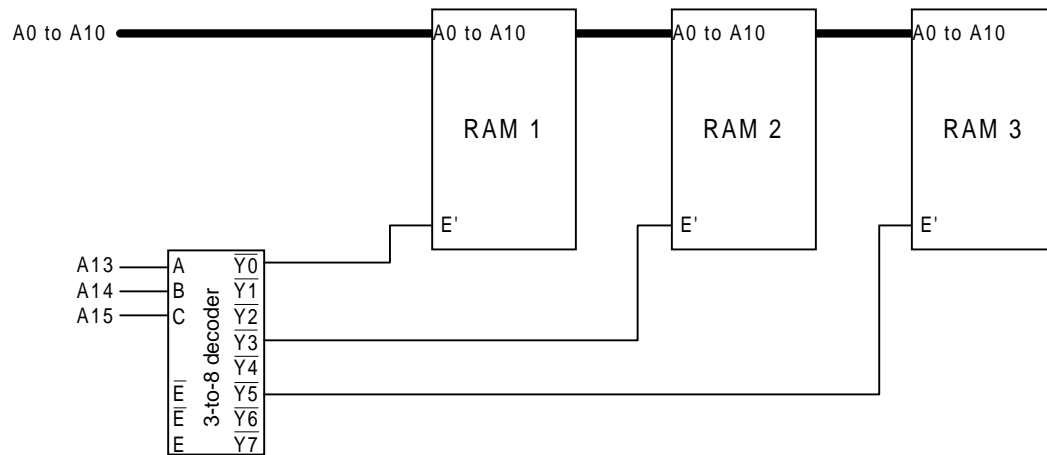4. Given the following circuit for a memory system: (a) what are the starting addresses for the three RAM chips? (b) List all the addresses that would access the third location of RAM 1.(5)



(a)


- ☞ 2 points for 0000, 6000, and A000 only.
- ☞ 2.5 points for all correct.

[illegible]

2.5 points for all four correct addresses.

[illegible]

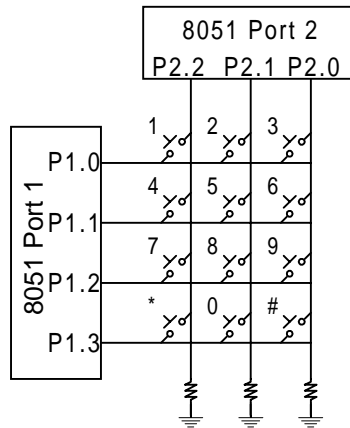5. Given a 3×4 matrix keypad (like the telephone keypad) and the connections for the keypad to the 8051 as shown below. Note that each intersection of a vertical and horizontal wire is not connected unless the corresponding key is pressed.



- Which port (P1 or P2) should be the input port and which should be the output port? (1)
- Which one of the following code segments will return the correct key pressed? (2)
  - P1 = 0x10;  
if(P2.2 == 0) return '1';
  - P2 = 0x06;  
if(P1.2 == 0) return '7';
  - P1 = 0x04;  
if(P2.1 == 1) return '8';
  - P2 = 0x04;  
if(P1.3 == 1) return '\*';
  - P1 = 0x06;  
if(P2.0 == 1) return '6';
- Write a segment of C code (no longer than 5 lines) that will determine that there is no key pressed and return a space (' '). (2)

### Answer

- a) P1 is the output port and P2 is the input port.

1 point for this

- b) ③

2 points for this

- c)

```
P1 = 0x0F;
if((P2.0 == 0) && (P2.1 == 0) && (P2.2 == 0)) return ' ';
```

2 points for this