

CS/EE 120B

Homework #1 Given 1/18/01. Due 1/25/01

32

1. Using D flip-flops and basic gates, design a counter that counts in the following sequence:

(8)

1, 5, 6, 1, 5, 6, 1, 5, ...

The contents of the flip-flops are the binary equivalent of the count.

Answer

The next-state and transition tables for the counter could be defined as:

Q_2	Q_1	Q_0	Next-state
0	0	1	1 0 1
1	0	1	1 1 0
1	1	0	0 0 1

The K-map for the next-state table is:

The next-state equations are:

$$D_2 = Q_{2(\text{next})} = Q_1'$$


$$D_1 = Q_{1(\text{next})} = Q_2 Q_1' \text{ or } Q_2 Q_0$$

$$D_0 = Q_{0(\text{next})} = Q_2' + Q_1$$

Q_2, Q_1	00	01	11	10
0	x x x	1 0 1	x x x	x x x
1	x x x	1 1 0	x x x	0 0 1

$Q_{2(\text{next})}, Q_{1(\text{next})}, Q_{0(\text{next})}$
Next-state map.



The schematic is as follows:

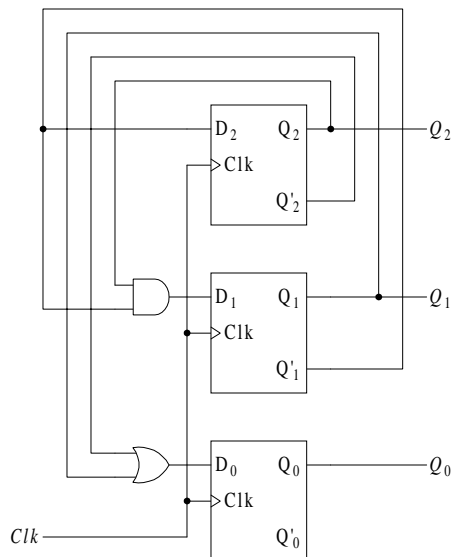


- ☞ 2 points for the next-state table.
- ☞ 2 points for the next-state equations.
- ☞ 4 points for getting the circuit correct.

Total 8 points.

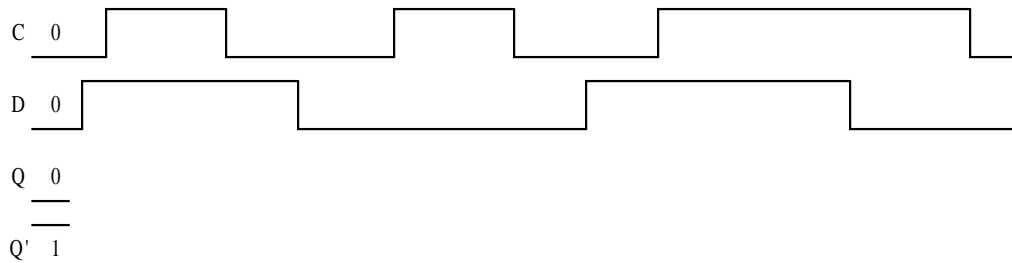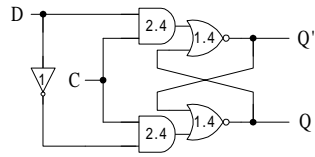2. Given the following circuit for the D latch, complete the Q and Q' timing trace below. The initial values of C , D , Q , and Q' are given in the trace. Clearly label the delay times for all the changes for Q and Q' on the trace. The numbers written inside each gate in the circuit is the delay time for that gate. (8)




Answer

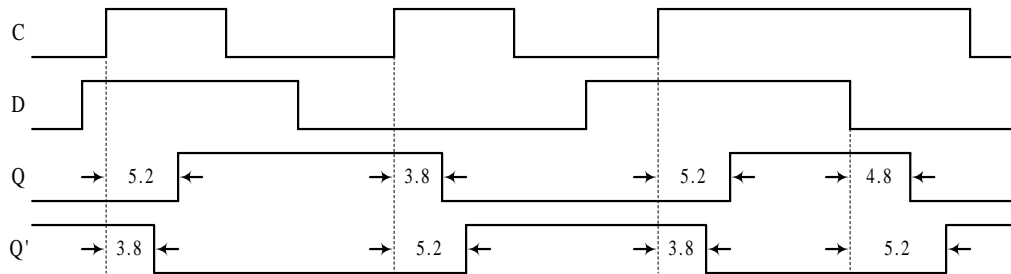

☞ 1 point each for getting one changing edge for Q or Q' and delay correct.

Total 8 points.

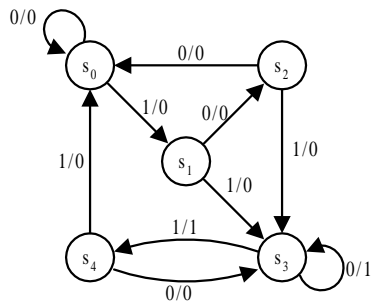3. For the state diagram below, derive one possible best state encoding using the minimum-bit-change heuristic. What is the total edge weight for your encoding? (8)



Answer

Note that the input/output values on the edges are not used in this heuristic.

One possible state encoding is as follows:

$$s_0 = 100$$

$$s_1 = 010$$

$$s_2 = 110$$


$$s_3 = 111$$

$$s_4 = 101$$

The total edge weight for this encoding is **10**.

Other encodings that will also give a total edge weight of 10:


s_0	100	101
s_1	000	001
s_2	001	000
s_3	010	011
s_4	110	111

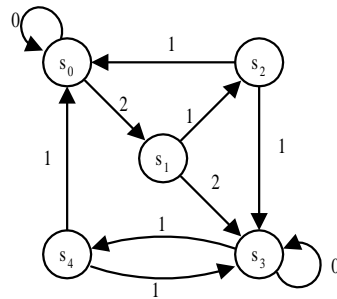

☞ 5 points for getting a total edge weight of 10.

☞ 3 points for getting a total edge weight of 11

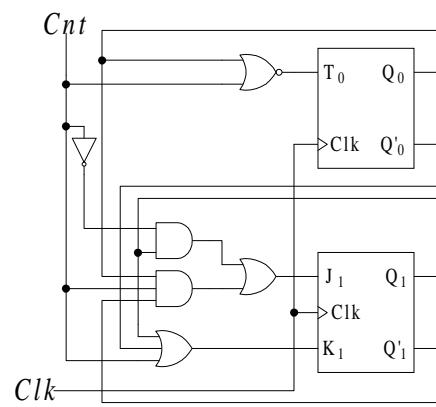4. Derive the state table and state diagram for the sequential circuit represented by the following schematic:



(8)

Answer

Step 1: The excitation equations are:

(2)

$$T_0 = (Cnt + Q_0)'$$

$$J_1 = Cnt'Q_1 + CntQ_1'Q_0$$

$$K_1 = Cnt + Q_1 + Q_0'$$

Step 2: The characteristic equation for the T flip-flop is:

$$Q_{next} = TQ' + TQ = T \oplus Q$$

The characteristic equation for the JK flip-flop is:

$$Q_{next} = K'Q + JQ'$$

The next-state equations are:

(2)

$$Q_{0next} = T_0 \oplus Q_0 = (Cnt + Q_0)' \oplus Q_0$$

$$= Cnt'Q_0' \oplus Q_0$$

$$Q_{1next} = K_1'Q_1 + J_1Q_1' = (Cnt + Q_1 + Q_0')'Q_1 + (Cnt'Q_1 + CntQ_1'Q_0)Q_1'$$

$$= Cnt'Q_1'Q_0Q_1 + Cnt'Q_1Q_1' + CntQ_1'Q_0$$

$$= 0 + 0 + CntQ_1'Q_0$$

Step 3a: The state table is:

(2)

Present State Q_1Q_0	Next State	
	$Q_{1next} Q_{0next}$	
	$Cnt = 0$	$Cnt = 1$
00	01	00
01	01	11
10	01	00
11	01	01

Step 3b: The state diagram is:

(2)

