

**UNIVERSITY OF CALIFORNIA, RIVERSIDE**  
**Department of Computer Science and Engineering**  
**Department of Electrical Engineering**  
**CS/EE120B – Introduction to Embedded Systems**  
**Midterm 1**  
**January 30, 2000**

30

**Name:** Solution Key **Student ID#:** \_\_\_\_\_

Please print legibly

**Lab Section:** 21 (WF 6-10): \_\_\_\_\_ 22 (MW 2-6): \_\_\_\_\_ 23 (TR 6-10): \_\_\_\_\_

(Numbers in parenthesis denote total possible points for question.)


1. Briefly describe the *metastable behavior* of a bistable element. (3)

**Answer**

A bistable element has three (3) equilibrium points – Two are stable and the third is metastable. When a circuit is operating at the metastable point, it could theoretically stay there indefinitely if there is no noise whatsoever. However, with a small amount of noise, it will drive the circuit toward one of the two stable points.


2. Use NAND gates and inverters to construct a D latch with active high enable, preset, and clear inputs. (5)

**Answer**

 


3. Complete the timing diagram below based on the following schematic


(6)

 

**Answer**

 

 4. Derive the next state table and state diagram for the sequential circuit represented by the following schematic: (8)



### Answer

Excitation equations:

$$\begin{aligned}
 T_0 &= (X \oplus Q_0)' = X'Q_0' + XQ_0 \\
 S_1 &= [(X \oplus Q_0)(X' + Q_1' + Q_0)]' \\
 &= (X \oplus Q_0)' + (X' + Q_1' + Q_0)' \\
 &= (X \oplus Q_0)' + (XQ_1Q_0') \\
 R_1 &= XQ_1Q_0'
 \end{aligned}$$

Characteristic equations:

$$\begin{aligned}
 Q_{0next} &= T_0 \oplus Q_0 \\
 Q_{1next} &= S_1 + R_1'Q_1
 \end{aligned}$$


Next state equations:

$$\begin{aligned}
 Q_{0next} &= T_0 \oplus Q_0 \\
 &= T_0Q_0' + T_0'Q_0 \\
 &= (X'Q_0' + XQ_0)Q_0' + (XQ_0' + X'Q_0)Q_0 \\
 &= X'Q_0' + X'Q_0 \\
 &= X' \\
 Q_{1next} &= S_1 + R_1'Q_1 \\
 &= (X \oplus Q_0)' + (XQ_1Q_0') + (XQ_1Q_0')'Q_1 \\
 &= X'Q_0' + XQ_0 + (XQ_1Q_0') + (X' + Q_1' + Q_0)Q_1 \\
 &= X'Q_0' + XQ_0 + (XQ_1Q_0') + X'Q_1 + Q_0Q_1
 \end{aligned}$$

Next state table:


Current State $Q_1Q_0$	Next State	
	$Q_{1next} Q_{0next}$	
	$X = 0$	$X = 1$
00	11	00
01	01	10
10	11	10
11	11	10

State diagram:

 

5. Synthesize a modulo-4 counter with a count enable input  $C$  and an output  $Y$  signal. The count is to be represented directly by the contents of two flip-flops; a JK flip-flop for the most significant bit and a T flip-flop for the least significant bit. Use the simple sequential binary encoding for the states. The counter counts when  $C$  is asserted and remains in the current state when  $C$  is de-asserted. The output  $Y$  is asserted when the count reaches 2 and the count enable input is enabled. Draw the synthesized circuit and complete the timing diagram below for the circuit.

(8)

 **Answer**