

CS120B – Homework #2


Given August 12, 2002. Due August 19, 2002 at the beginning of class.

Use the datapath and functional operations shown in Figure 1 below to implement the following algorithm:

Input a number n and output the factorial of n , i.e. $n!$ Assume that n is small and no overflow error results from the calculations.

You need to do the following:

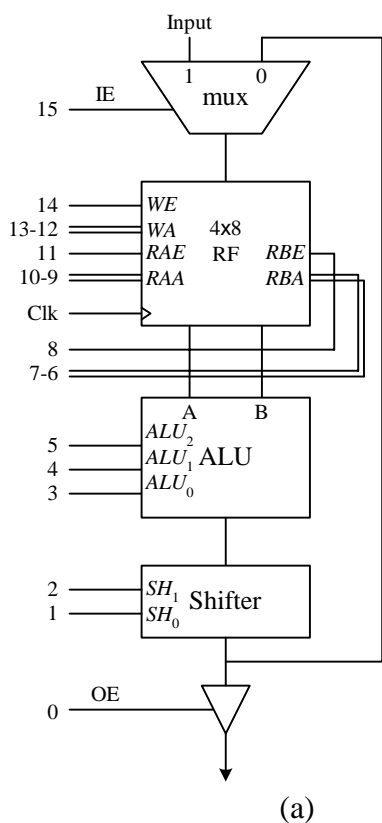- Write the high-level pseudo-code to implement the algorithm. (2)
- Convert the pseudo-code to control words. (2)
- Draw the state-diagram for the control words. (2)
- Derive the next-state table. (2)
- Derive the next-state equations. (2)
- Derive the output equations. (2)
- Draw the complete FSM circuit. (2)
- Draw the circuit(s) that generates signals from the datapath for the FSM. (2)



ALU_2	ALU_1	ALU_0	Operation
0	0	0	Pass through A
0	0	1	$A \text{ AND } B$
0	1	0	$A \text{ OR } B$
0	1	1	NOT A
1	0	0	$A + B$
1	0	1	$A - B$
1	1	0	$A + 1$
1	1	1	$A - 1$

(b)

SH_1	SH_0	Operation
0	0	Pass through
0	1	Shift left
1	0	Shift right
1	1	Rotate right

(c)

Figure 1. 8-bit datapath with register file: (a) circuit; (b) ALU operations; (c) Shifter operations.