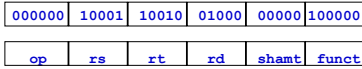


## Control

- Selecting the operations to perform (ALU, read/write, etc.)
- Controlling the flow of data (multiplexor inputs)
- Information comes from the 32 bits of the instruction
- Example:


add \$8, \$17, \$18      Instruction Format:



- ALU's operation based on instruction type and function code
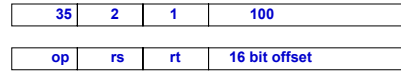
## Control

- e.g., what should the ALU do with this instruction
- Example: lw \$1, 100(\$2)



- ALU control input

000	AND
001	OR
010	add
110	subtract
111	set-on-less-than


- Multi-level control is common: main control unit generates ALUop (load/store, branch, arithmetic) bits, which are then used as input to the ALU control that generates the actual signals (3 bits shown above) to control the ALU unit

## Control


- Must describe hardware to compute 3-bit ALU control input
  - given instruction type
    - 00 = lw, sw
    - 01 = beq,
    - 10 = arithmetic
- Describe it using a truth table (can turn into gates):

ALUOp		Funct field					Operation	
ALUOp1	ALUOp0	F5	F4	F3	F2	F1	F0	
0	0	X	X	X	X	X	X	010
X	1	X	X	X	X	X	X	110
1	X	X	X	X	0	0	0	010
1	X	X	X	X	0	0	1	110
1	0	X	X	X	0	1	0	000
1	X	X	X	X	0	1	0	001
1	X	X	X	X	1	0	1	111

## ALU Control Schematic Diagram

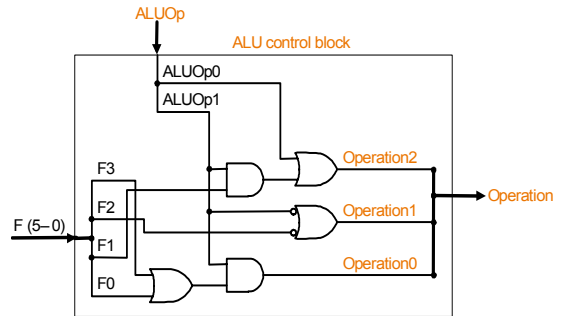

## Control

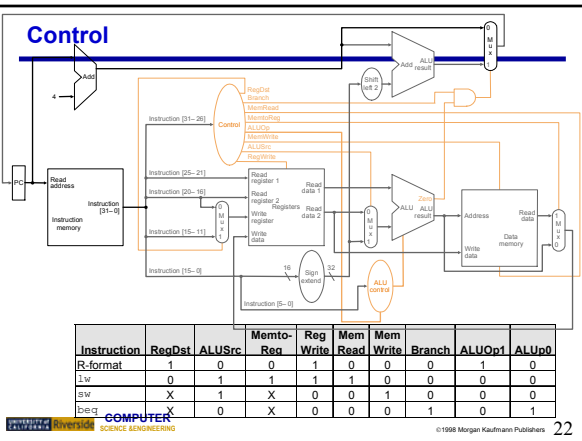

## Recall Instruction Format

R	op	rs	rt	rd	shamt	funct
	31-26	25-21	20-16	15-11	10-6	5-0
I	op	rs	rt	16 bit address		
	31-26	25-21	20-16	15-0		
J	op	26 bit address				
	31-26	25-0				

## Main Control Schematic Diagram

