

# UCR

## CS161 – Design and Architecture of Computer Systems

### Single Cycle CPU Design

UNIVERSITY OF CALIFORNIA, RIVERSIDE

# CPU Organization



- We will build a CPU to implement our subset of the MIPS ISA
  - Memory Reference Instructions:
    - Load Word (LW)
    - Store Word (SW)
  - Arithmetic and Logic Instructions:
    - ADD, SUB, AND, OR, SLT
  - Branch and Jump Instructions:
    - Branch if equal (BEQ)
    - Jump unconditional (J)
- These basic instructions exercise a majority of the necessary datapath and control logic for a more complete implementation


# Generic Implementation

- › Use program counter (PC) to supply instruction address
- › Get instruction from memory
- › Read registers
- › Use instruction to decide exactly what to do


# CPU Implementations

- ▶ Single-cycle CPU (CPI = 1)
  - ▶ All instructions execute in a single, long clock cycle
  
- ▶ Multi-cycle CPU (CPI = n)
  - ▶ Instructions can take a different number of short clock cycles to execute

# Single-Cycle Datapath

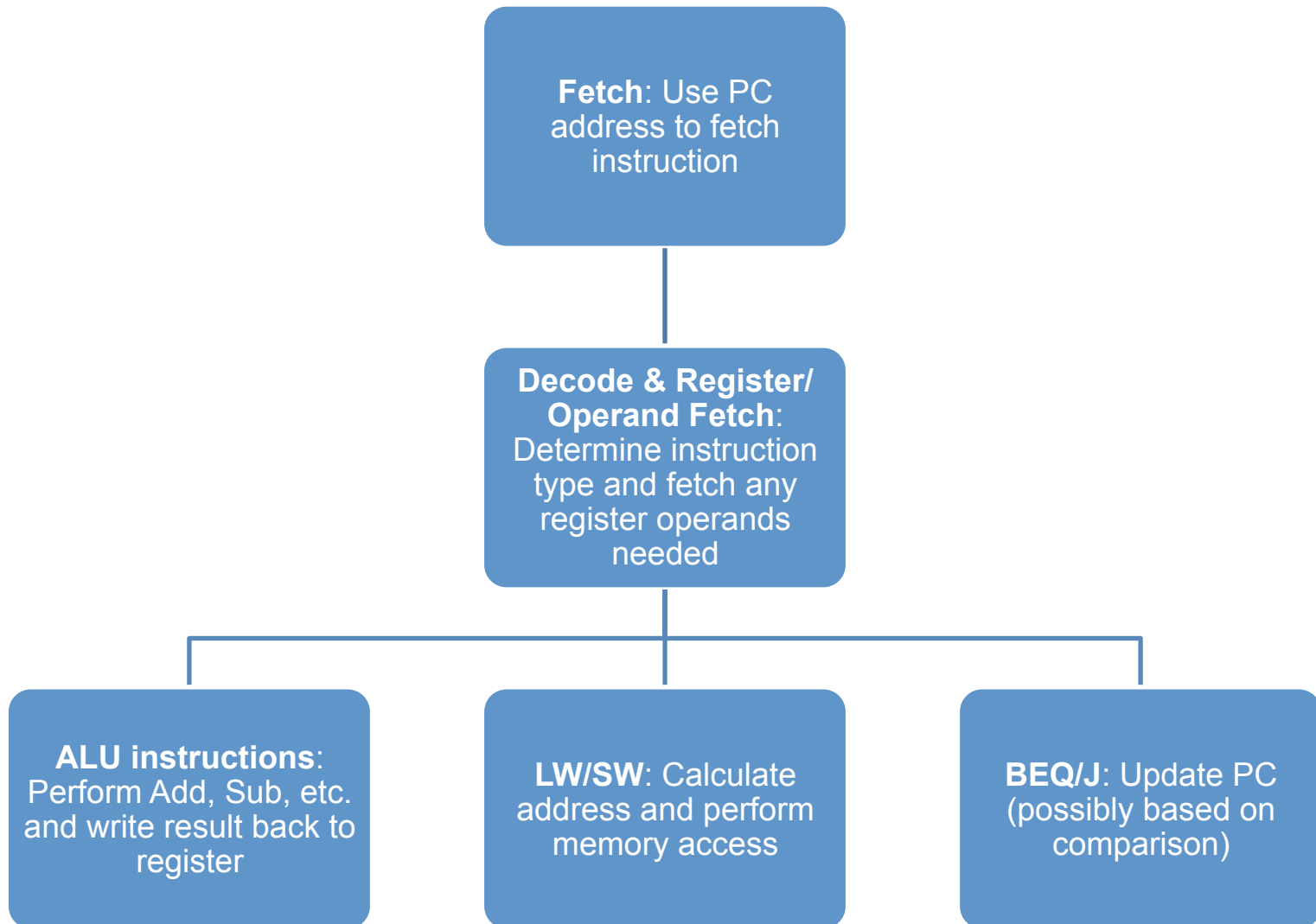


# Abstract/Simplified View

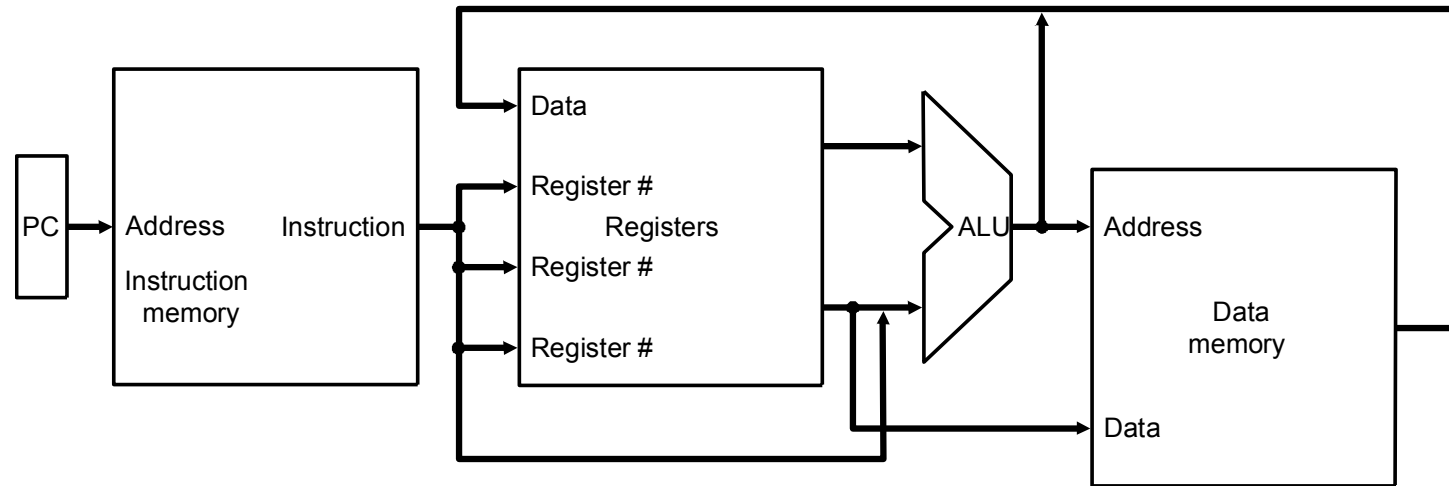

- Two types of functional units:
  - Elements that operate on data values (combinational)
  - Elements that contain state (sequential)

 
# State Elements

- › Unclocked vs clocked
- › Clocks used in synchronous logic


 
# Unclocked State Element

- ▶ Set-reset latch
  - ▶ Output depends on present inputs and also on past inputs







# Latches and Flip-flops

- › Output is equal to the stored value inside the element (don't need to ask for permission to look at the value)
- › Change of state (value) is based on the clock
- › Latches: whenever the inputs change, and the clock is asserted
- › Flip-flop: state changes only on a clock edge (edge-triggered methodology)

 
 
# D-latch

- > Two inputs:
  - > the data value to be stored (D)
  - > the clock signal (C) indicating when to read & store D
- > Two outputs:
  - > the value of the internal state (Q) and it's complement




# D flip-flop (Register)

- Output changes only on the clock edge

 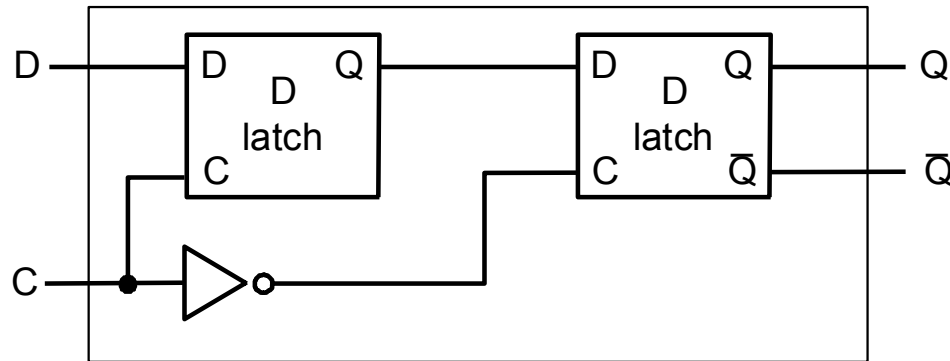


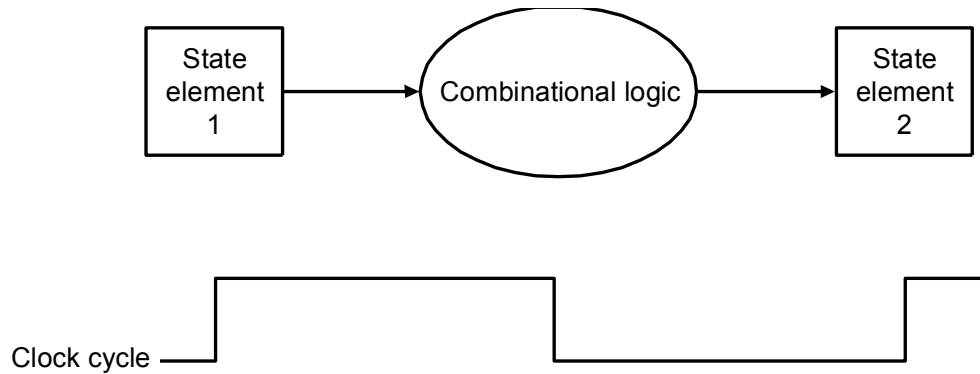
# Our Implementation

- › An edge triggered methodology
- › Typical execution:
  - › Read contents of some state elements,
  - › Send values through some combinational logic
  - › Write results to one or more state elements





# Register File

- Built using D flip-flops

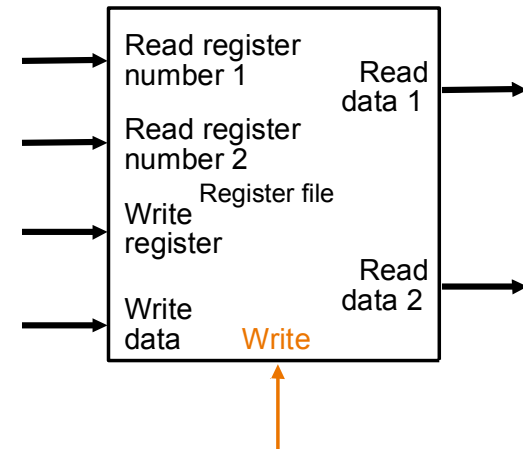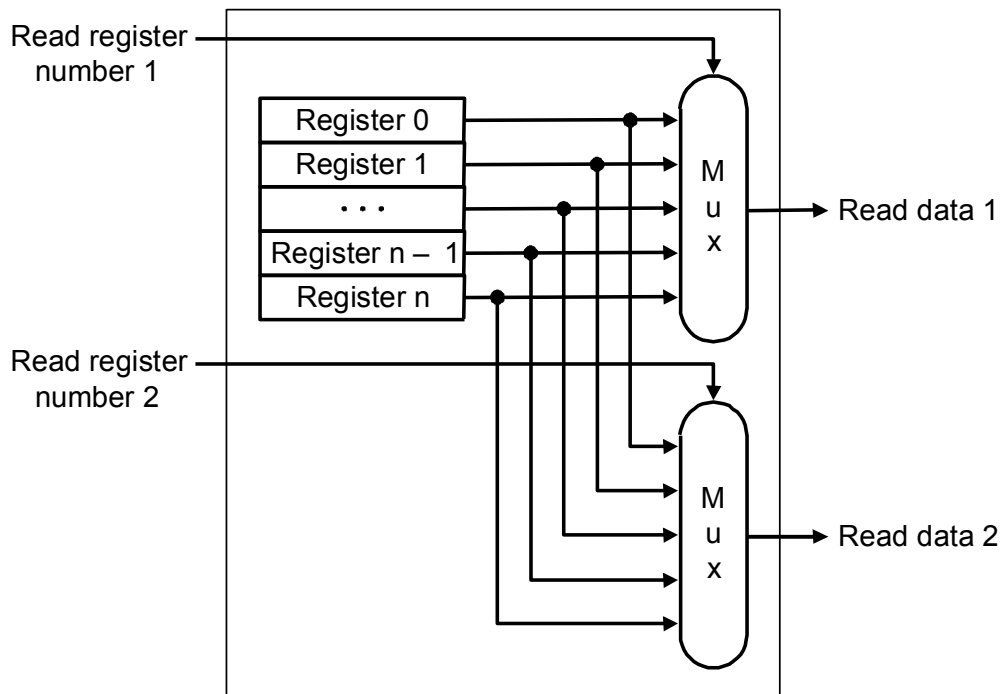

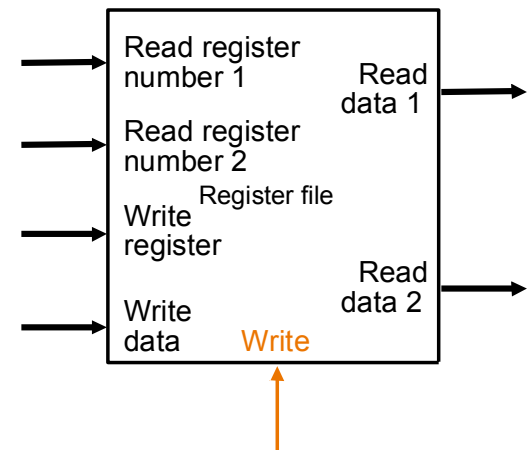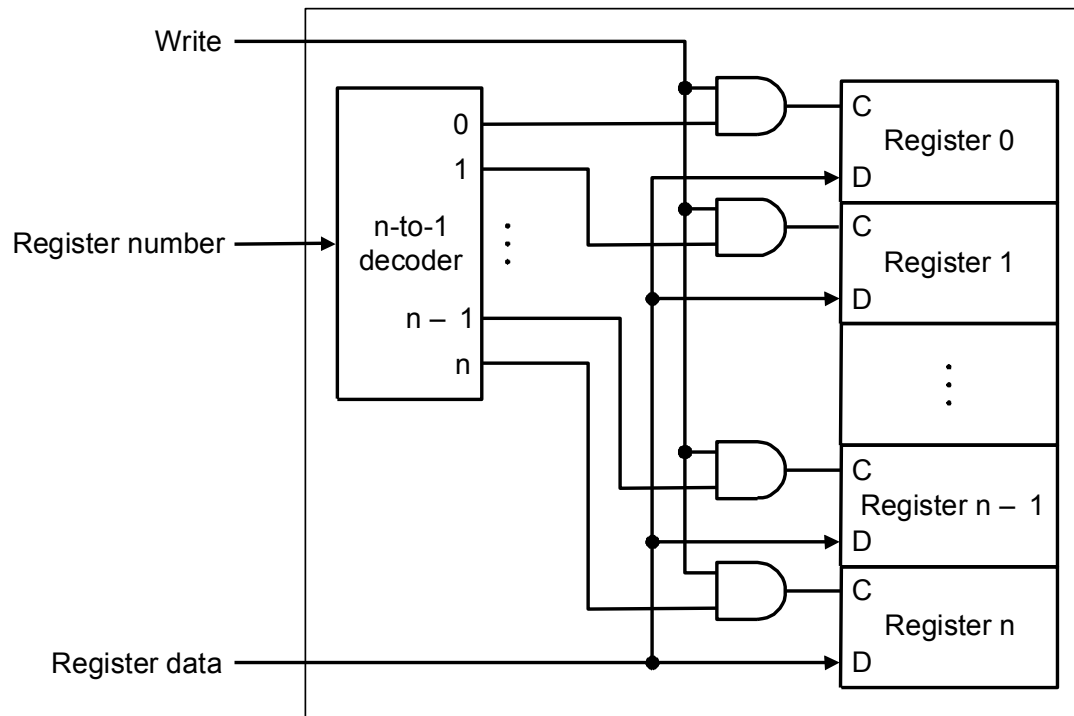
# Register File

- ▶ Note: We still use the real clock to determine when to write



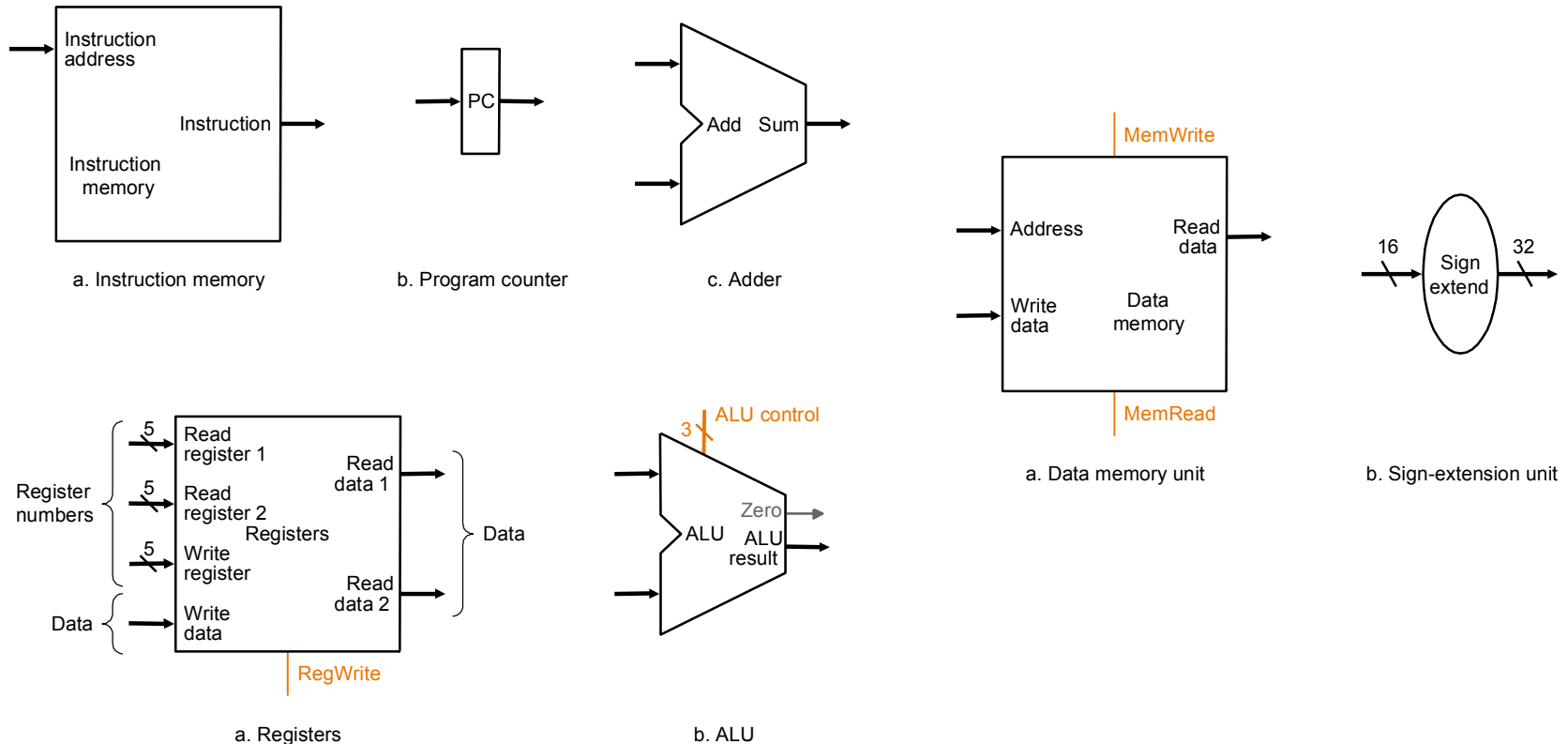
# Simple Implementation

- Include the functional units we need for each instruction
- Think of this as a puzzle! 😊


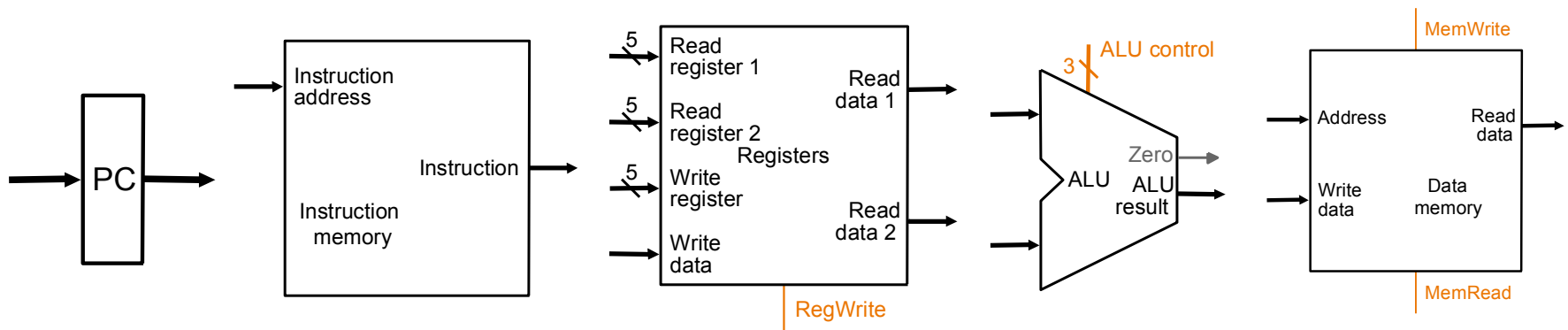
# Instruction Ordering

- Identify which components each instruction type would use and in what order: ALU-Type, LW, SW, BEQ



ALU-Type  
(ADD R3, R2, R1)

1. PC
2. I-Mem
3. Registers
4. ALU
5. WB to Reg.

LW  
(LW R2, 4(R1))

1. PC
2. I-Mem
3. Base. Reg.
4. ALU
5. Read Mem
6. WB to Reg.

SW  
(SW R2, 8(R1))

1. PC
2. I-Mem
3. Base. Reg
4. ALU
5. Write Mem


BEQ  
(BEQ R3, R1, displace)

1. PC
2. I-Mem
3. Register Access
4. Compare
5. If Zero,  
Update PC = PC+disp



 
# Fetch Components

- › Required operations
  - › Taking address from PC and reading instruction from memory
  - › Incrementing PC to point at next instruction
- › Components
  - › PC register
  - › Instruction Memory / Cache
  - › Adder to increment PC value



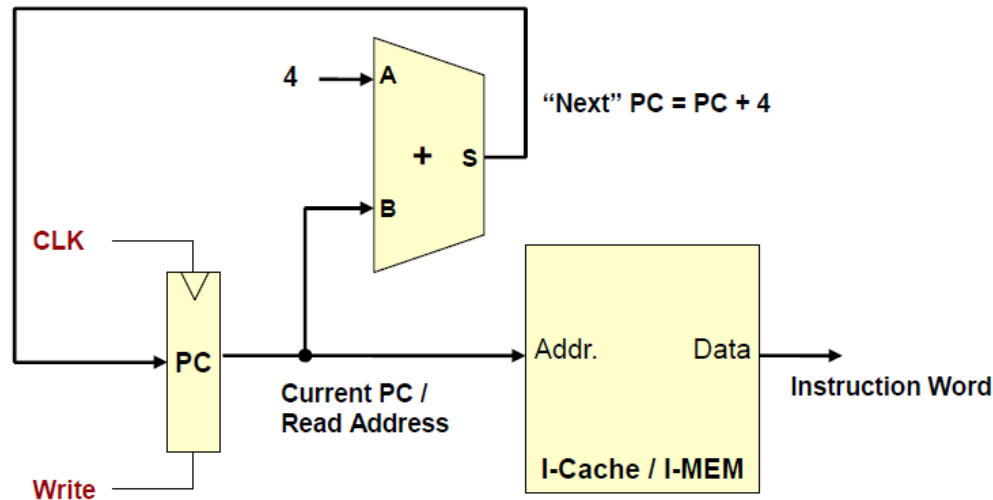
# Fetch Datapath

- PC value serves as address to instruction memory while also being incremented by 4 using the adder
- Instruction word is returned by memory after some delay
- New PC value is clocked into PC register at end of clock cycle



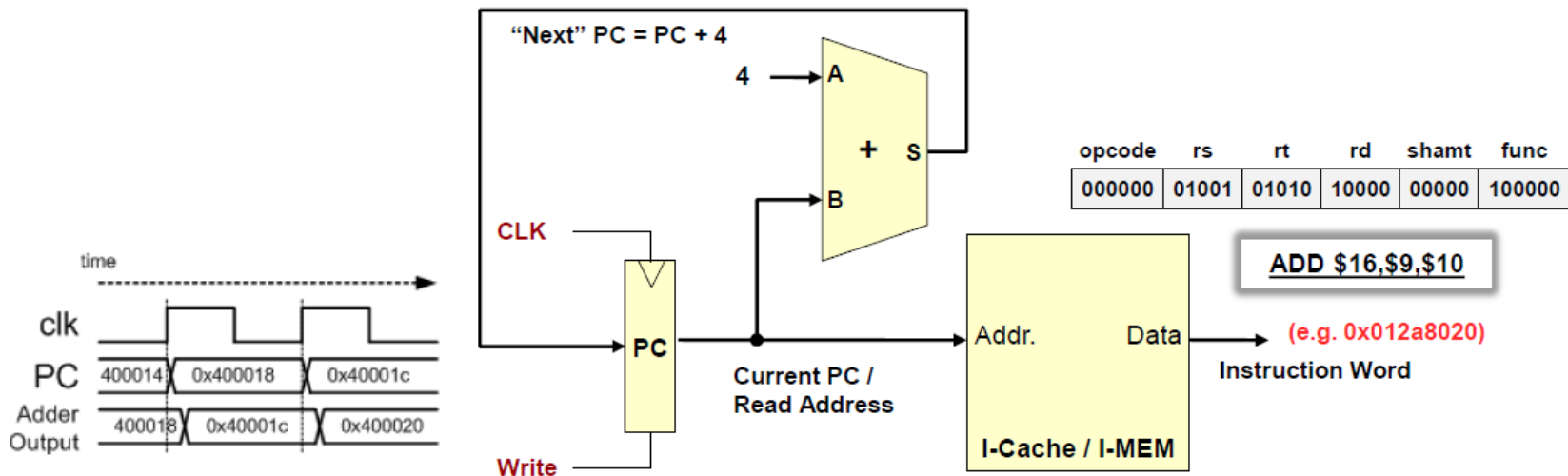
# Fetch Datapath Example

- ▶ The PC and adder operation is shown
  - ▶ The PC doesn't update until the end of the current cycle
- ▶ The instruction being read out from the instruction memory
  - ▶ We have shown "assembly" syntax and the field by field machine code breakdown




# Modified Fetch Datapath

- Support for branch instruction added

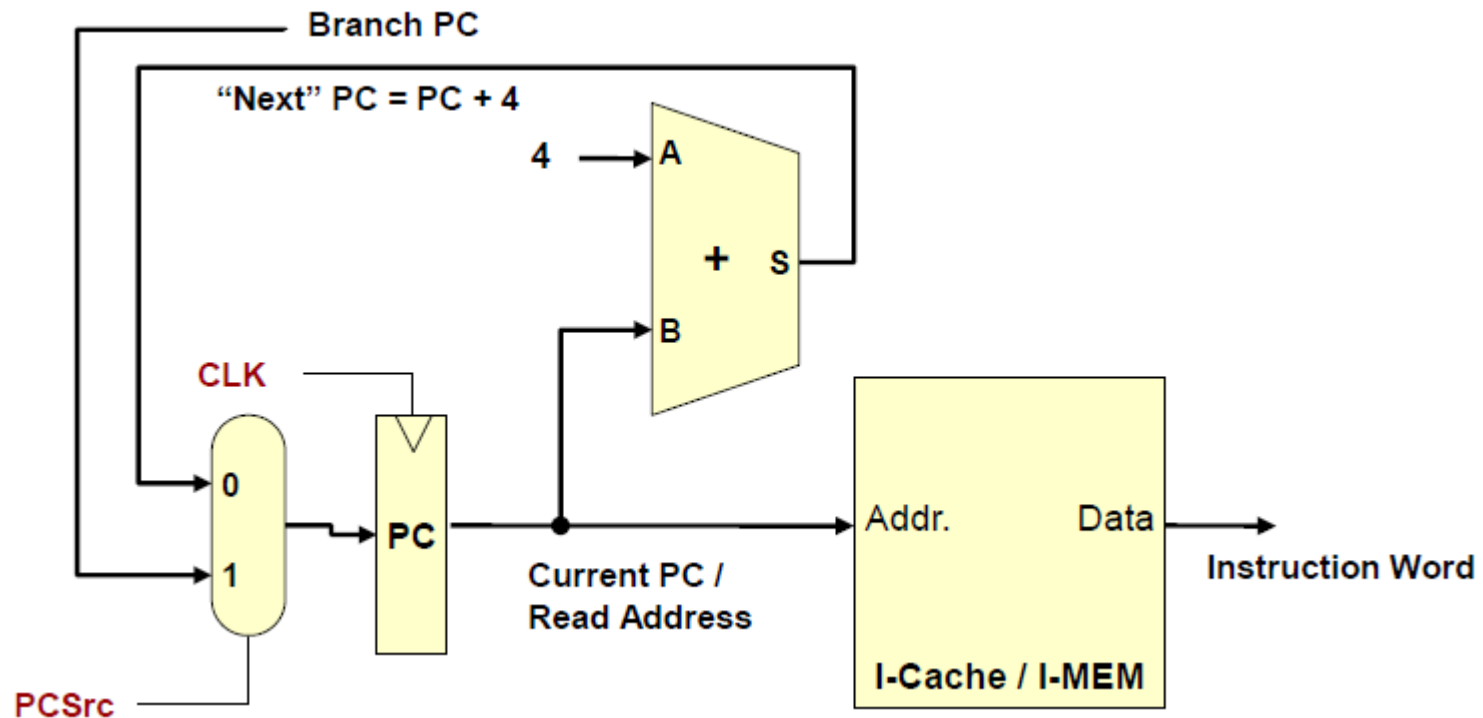

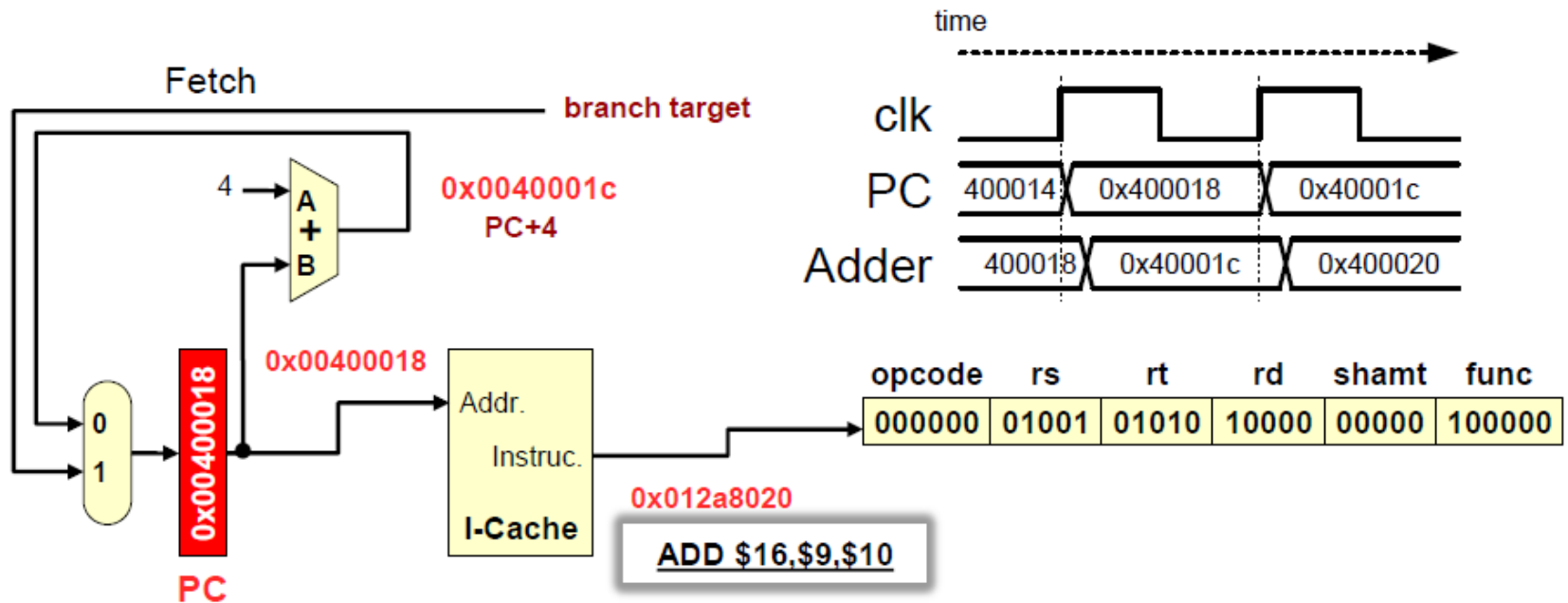
# Modified Fetch Example

- Mux provides a path for branch target address



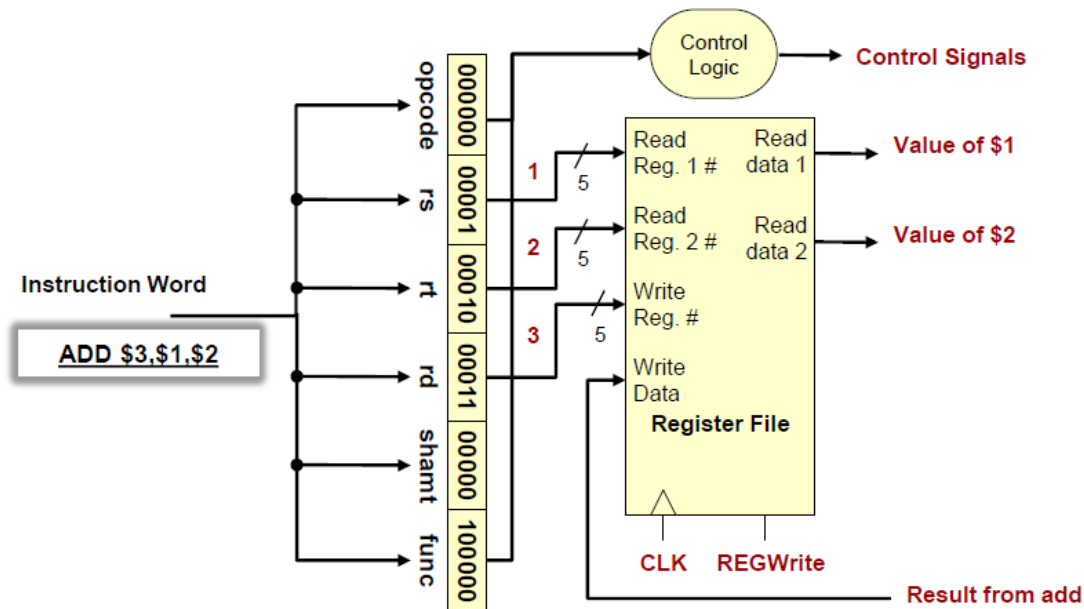
# Decode

- › Opcode and func. field are decoded to produce other control signals
- › Execution of an ALU instruction (ADD \$3,\$1,\$2) requires reading 2 register values and writing the result to a third
- › REGWrite is an enable signal indicating the write data should be written to the specified register



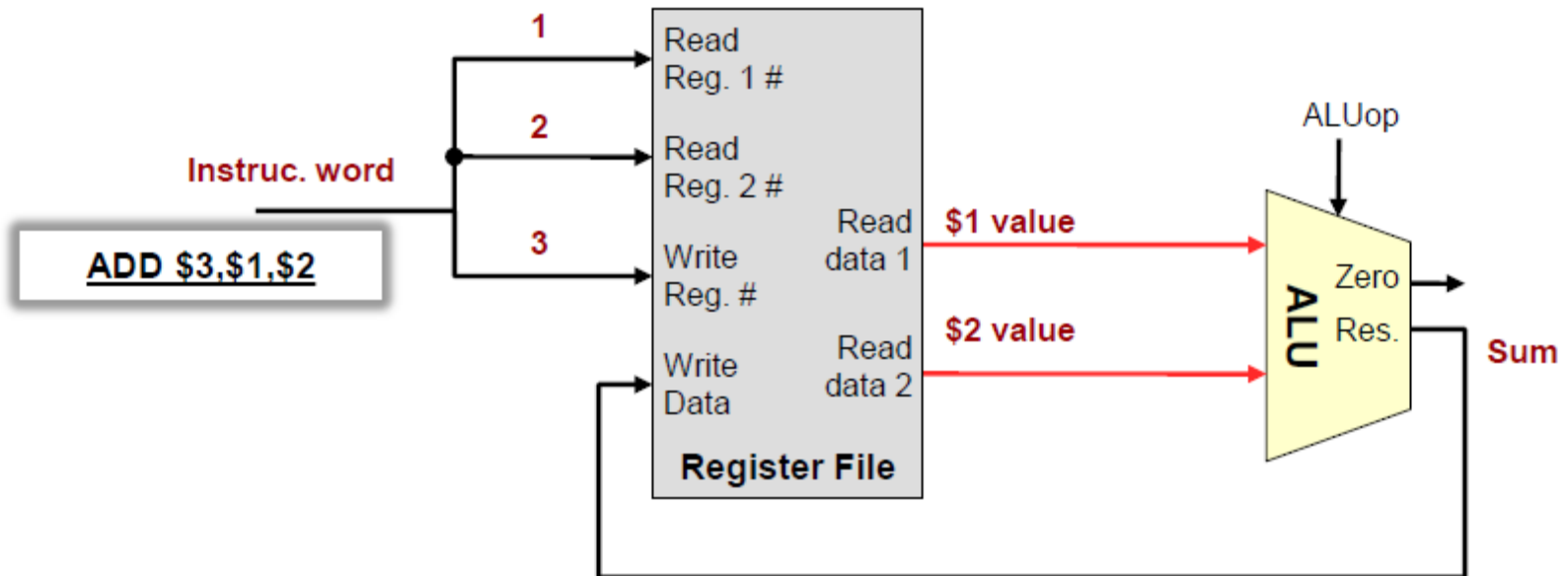
# ALU Datapath

- ▶ ALU takes inputs from register file and performs the add, sub, and, or, slt operations
- ▶ Result is written back to dest. register


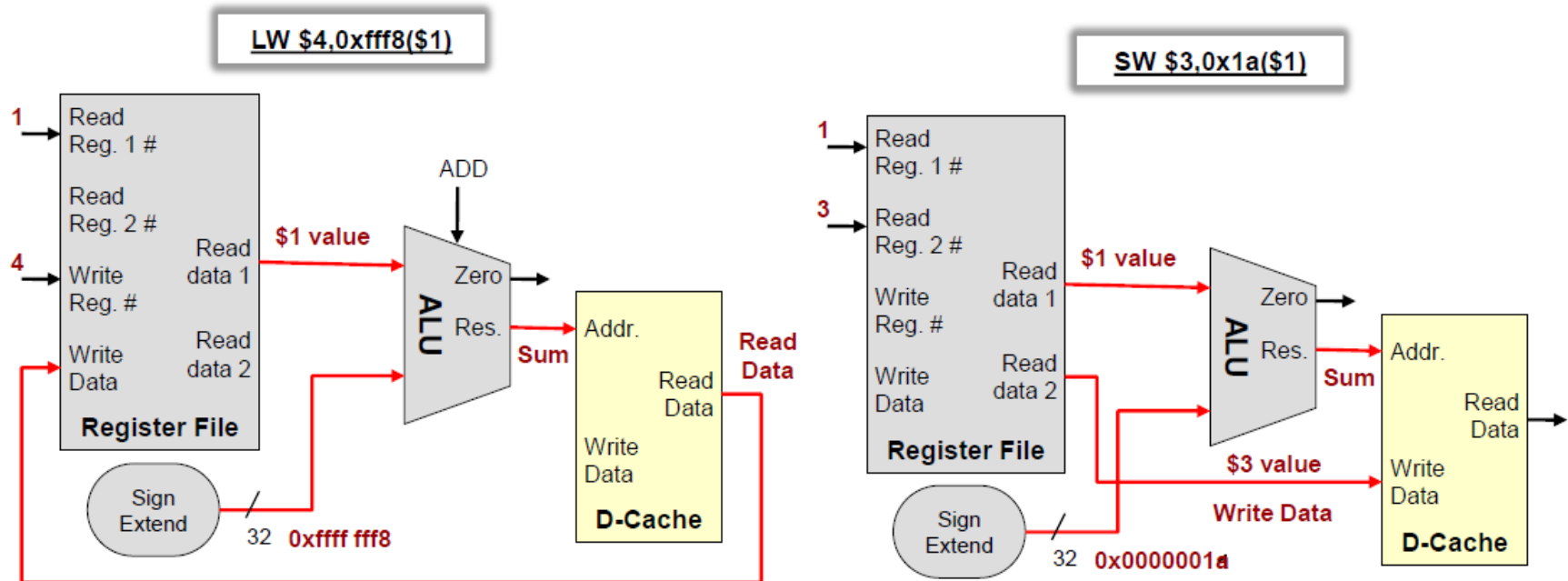
# Memory Access Datapath


- › Operands are read from register file while offset is sign extended
- › ALU calculates effective address
- › Memory access is performed
- › If LW, read data is written back to register






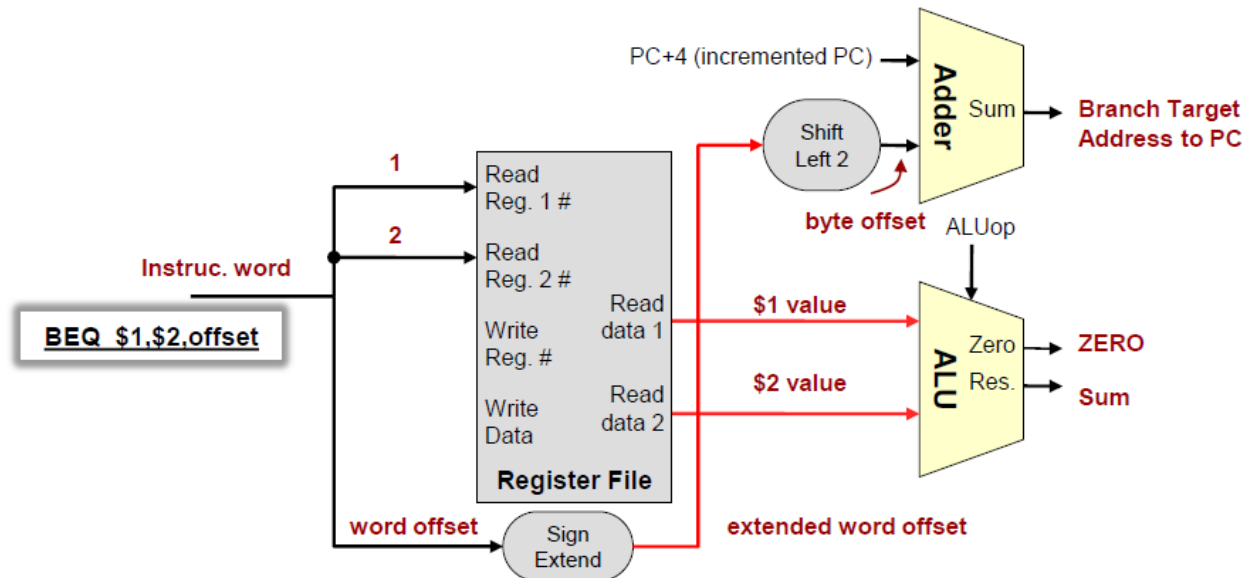
# Branch Datapath

- BEQ requires...
  - ALU for comparison (examine 'zero' output)
  - Sign extension unit for branch offset
  - Adder to add PC and offset
    - Need a separate adder since ALU is used to perform comparison



  
# Memory Access


- LW and SW require:
  - Sign extension unit for address offset
  - ALU to compute (add) base address + offset
  - Data memory



Sign Extension Unit

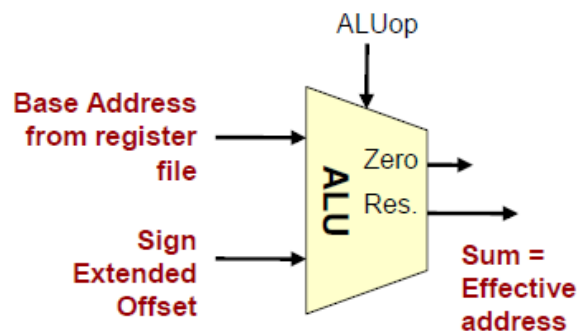

ALU (Adder)

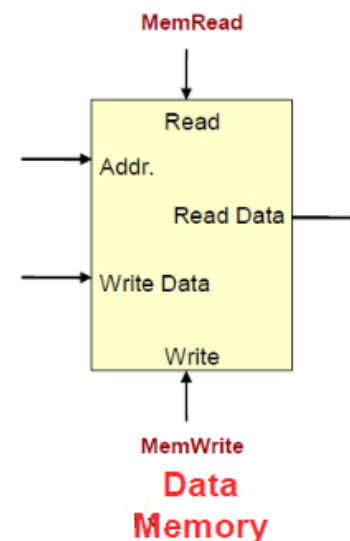


MemWrite  
Data Memory

# Combining Datapaths

- › Combine all datapaths into one
- › We can have multiple options for certain inputs
- › Use muxes to select appropriate input for a given instruction
- › Generate control bits to control mux

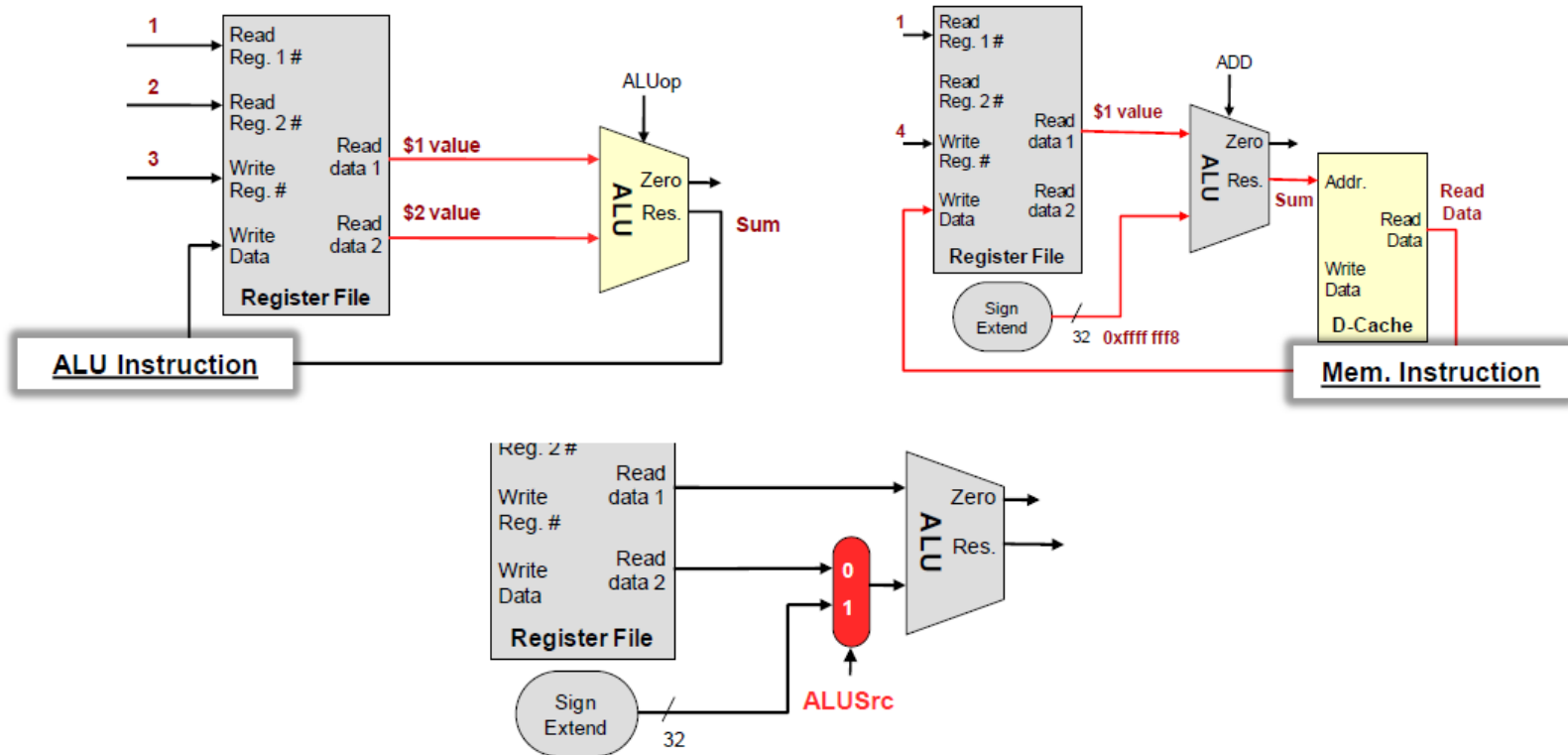
# ALUSrc Mux

- Mux controlling second input to ALU
  - ALU instruction provides Read Register 2 data to the 2nd input of ALU
  - LW/SW uses 2nd input of ALU as an offset to form effective address



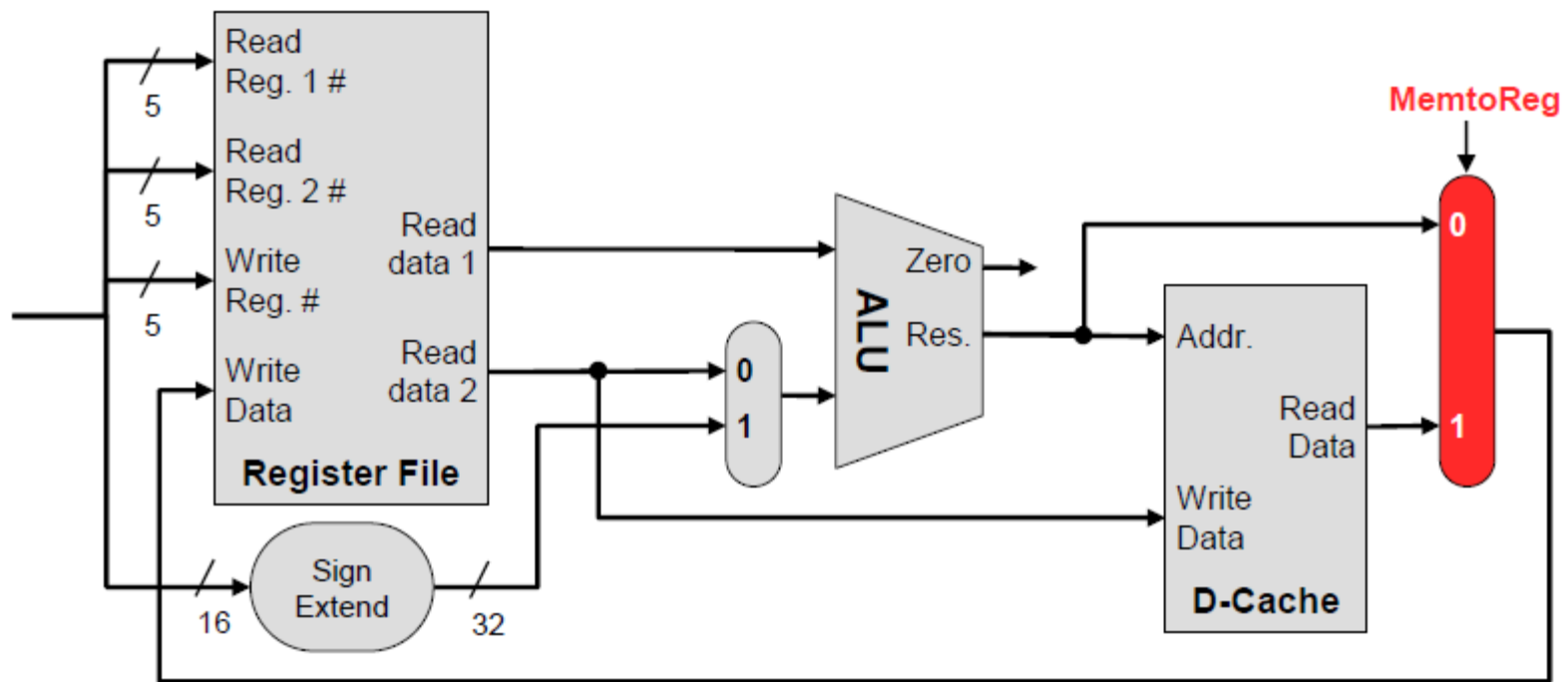
# MemtoReg Mux

- Mux controlling writeback value to register file
  - ALU instructions use the result of the ALU
  - LW uses the read data from data memory



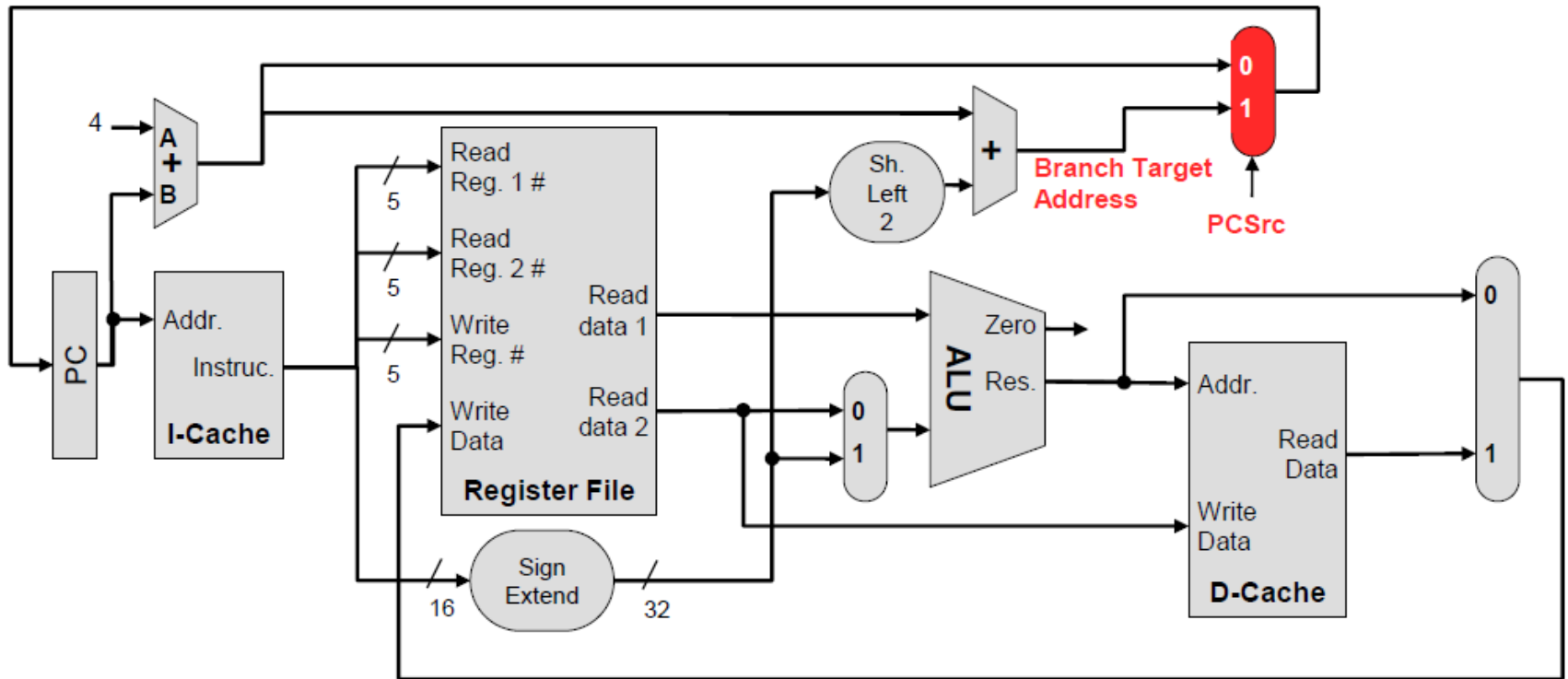
# PCSrc Mux

- Next instruction can either be PC+4, or the branch target address, PC+Offset



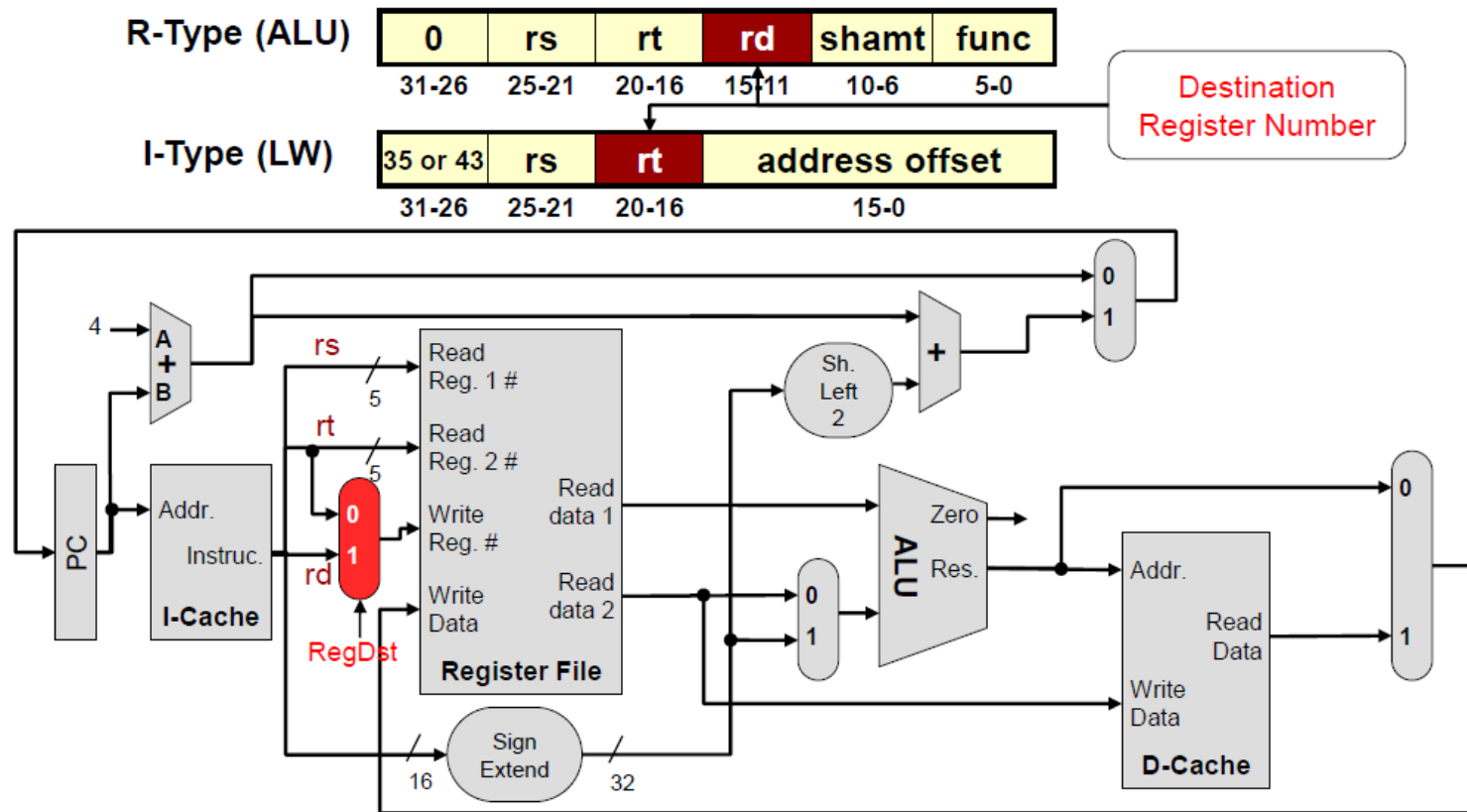
# RegDst Mux

- Different destination register ID fields for ALU and LW instructions



# Single Cycle CPU Datapath

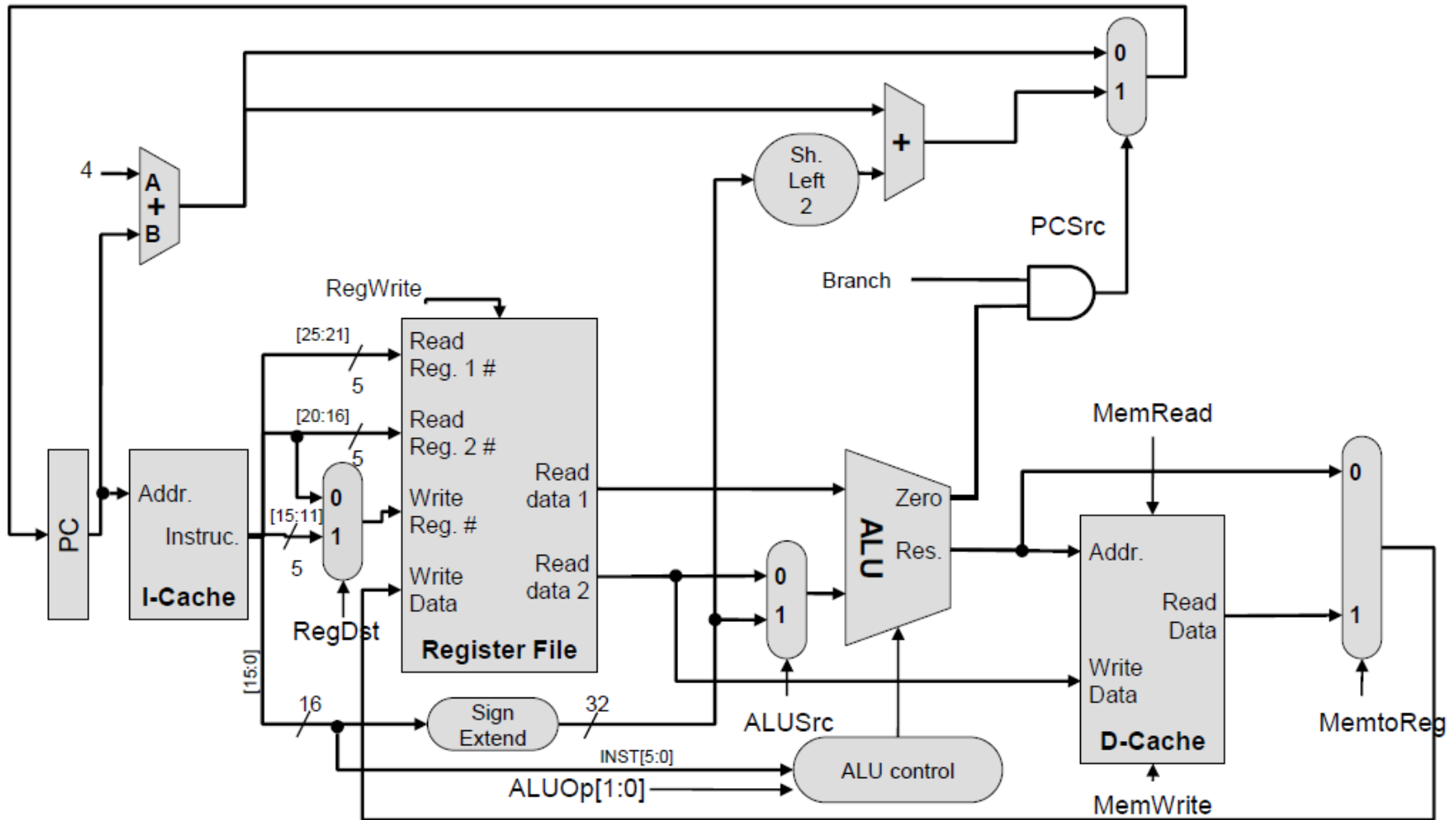




# Control

- We now have data path in place, but how do we control which path an instruction will take?
- Single-Cycle Design:
  - Instruction takes exactly one clock cycle
  - Datapath units used only once per cycle
  - Writable state updated at end of cycle
- What must be “controlled”?
  - Muxes
  - Writeable state elements: RF, Mem
  - ALU

# Control


- > Single-Cycle Design: everything happens in one clock cycle
  - > until next falling edge of clock, processor just one big combinational circuit!!!
  - > control is just a combinational circuit (output, just function of inputs)
- > outputs? control points in datapath
- > inputs? the current instruction! (opcode, funct control everything)

# Datapath + Control

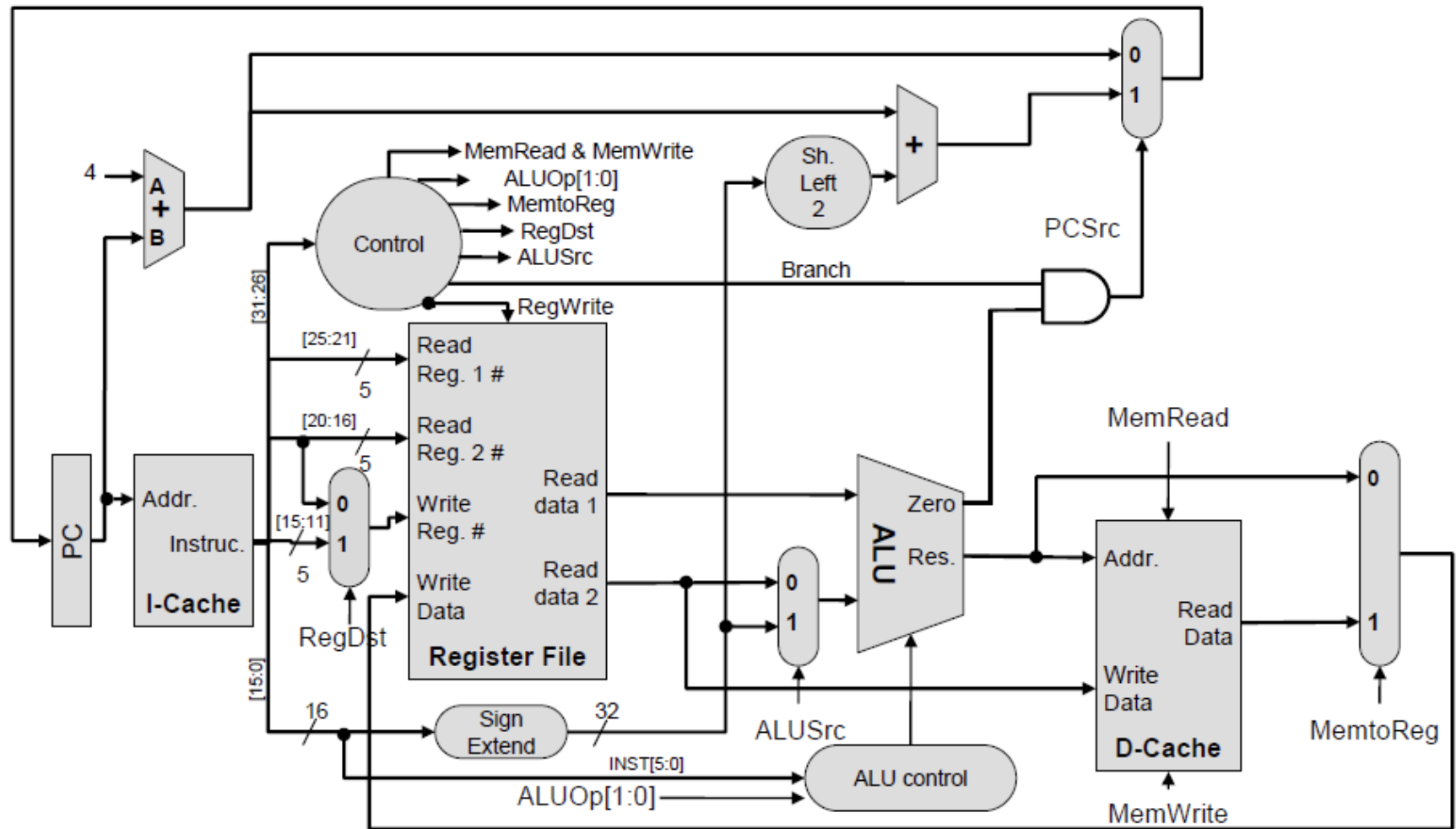

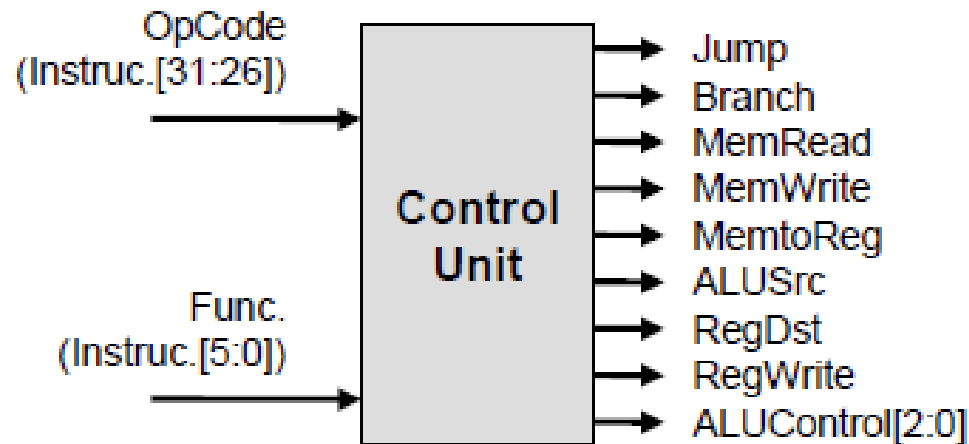
# Defining Control

- ▶ Most control signals are a function of the opcode (i.e. LW/SW, R-Type, Branch, Jump)


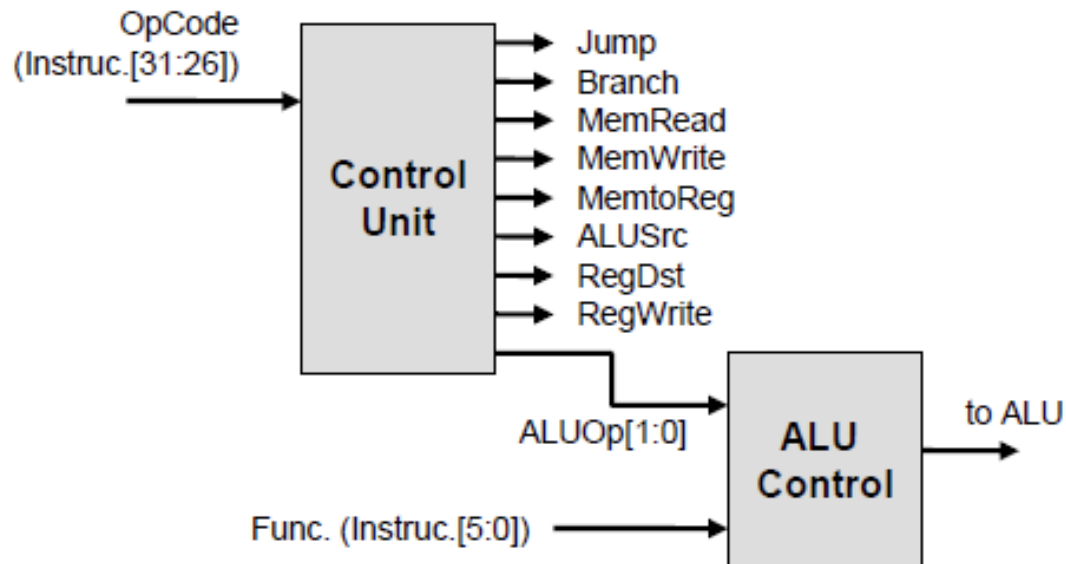
# Defining Control

- ▶ Funct field only present in R-type instruction
  - ▶ Funct controls ALU only
- ▶ To simplify control, define Main and ALU control separately




# ALU Control


- ALU Control needs to know what instruction type it is:
  - R-Type (op. depends on func. code)
  - LW/SW (op. = ADD)
  - BEQ (op. = SUB)
- Let main control unit produce ALUOp[1:0] to indicate instruction type, then use function bits if necessary to tell the ALU what to do

Instruction	ALUOp[1:0]
LW/SW	00
Branch	01
R-Type	10

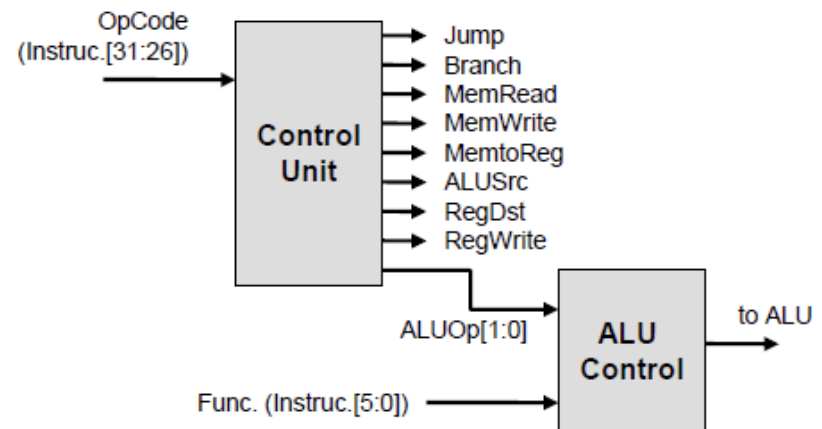Control unit maps instruction opcode to ALUOp[1:0] encoding



# ALU Control

 

Note: We don't use NOR.  
Ignore MSB in ALUCon.

ALUCon	ALU function	Instruction supported
0000	AND	R-format (AND)
0001	OR	R-format (OR)
0010	Add	R-format (Add), lw, sw
0110	Subtract	R-format (Sub), beq
0111	Set on less than	R-format (SlT)
1100	NOR	R-format (Nor)

# ALU Control Truth Table



- › ALUControl[2:0] is a function of ALUOp[1:0] and Func[5:0]

Instruc.	Instruction Operation	Desired ALU Action	ALUOp[1:0]	Func[5:0]	ALUControl
LW	Load Word	Add	00	X	010
SW	Store Word	Add	00	X	010
Branch	BEQ	Subtract	01	X	110
R-Type	AND	And	10	100100	000
R-Type	OR	Or	10	100101	001
R-Type	Add	Add	10	100000	010
R-Type	Sub	Subtract	10	100010	110
R-Type	SLT	Set on less than	10	101010	111




# Simplified ALUControl Truth Table

- › We can simplify using don't cares
- › Can turn into gates


ALUOp		Funct Field						ALUCont.
ALUOp1	ALUOp0	F5	F4	F3	F2	F1	F0	
0	0	X	X	X	X	X	X	010
X	1	X	X	X	X	X	X	110
1	X	X	X	0	0	0	0	010
1	X	X	X	0	0	1	0	110
1	X	X	X	0	1	0	0	000
1	X	X	X	0	1	0	1	001
1	X	X	X	1	0	1	0	111

- ›  $ALUControl2 = ALUOp0 \text{ OR } (ALUOp1 \text{ AND } F1)$
- ›  $ALUControl1 = ALUOp1 \text{ NOR } F2$
- ›  $ALUControl0 = ALUOp1 \text{ AND } (F3 \text{ OR } F0)$

# Fully Minimized ALU Control

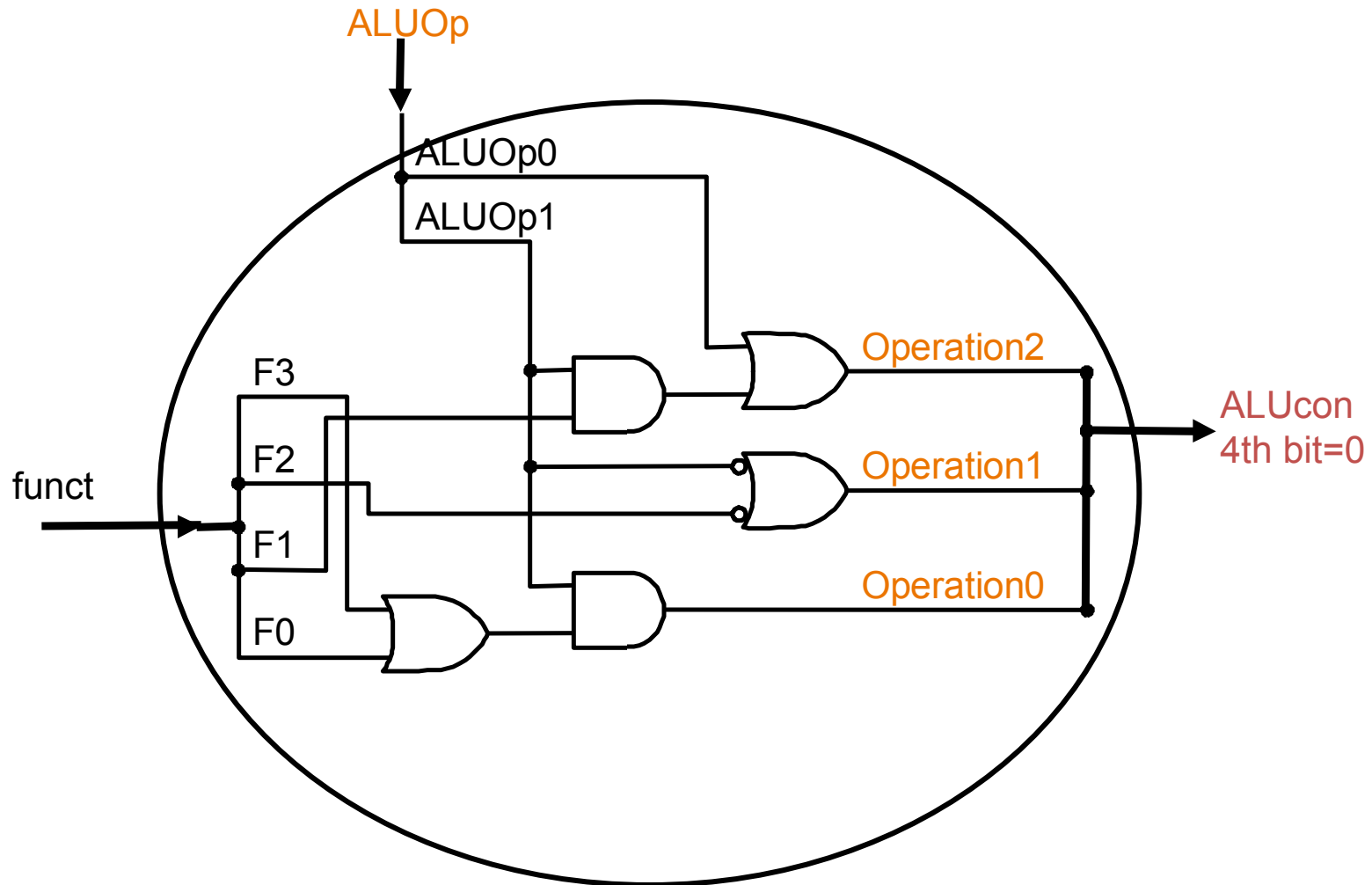


# Datapath + Control

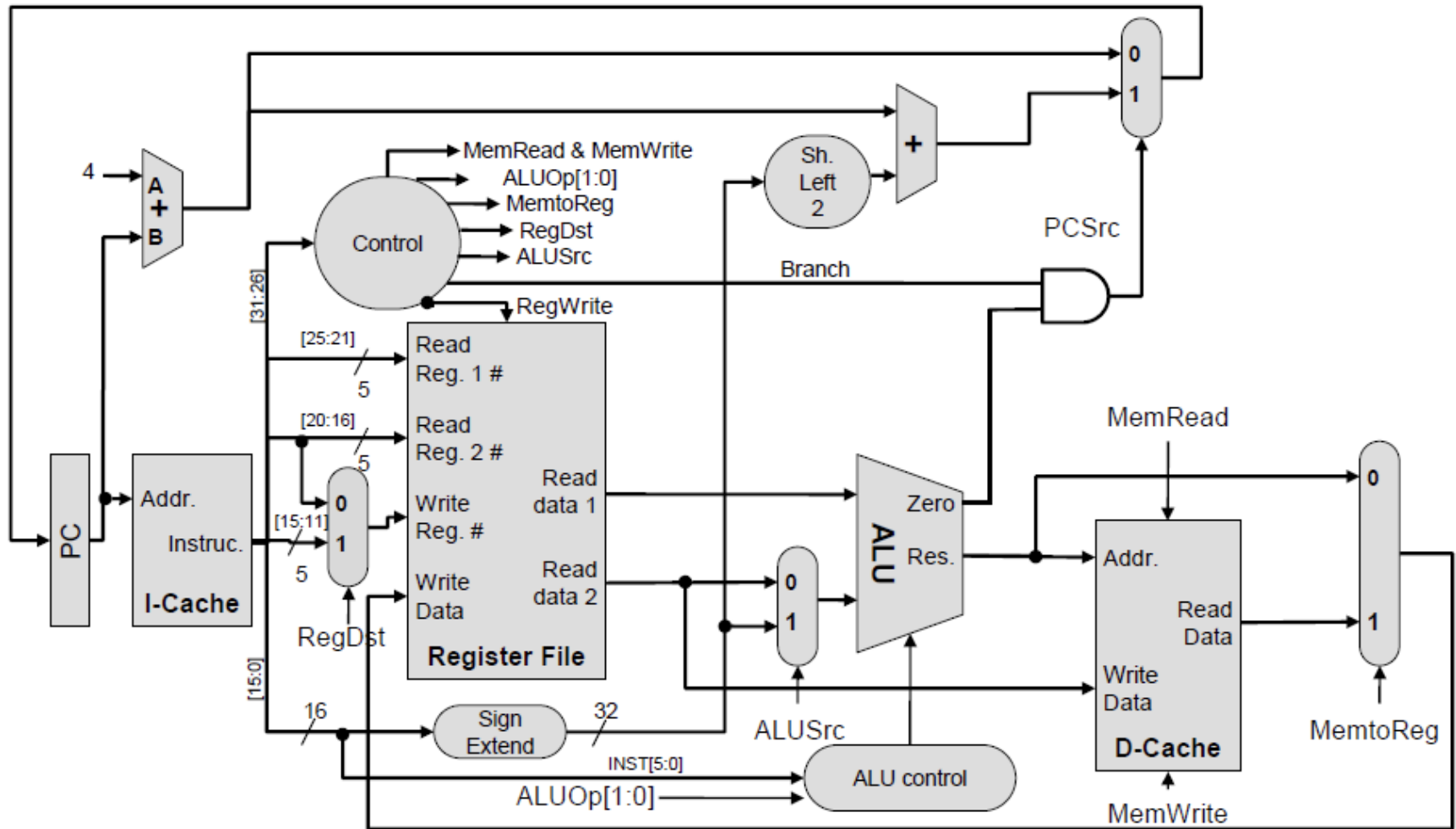

 
# Main Control Signals

- › Main control signals are function of opcode




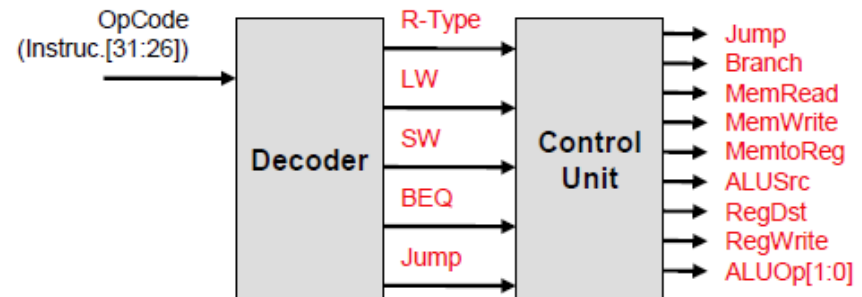Could generate each control signal by writing full truth table of the 6-bit opcode




Simpler for humans to design if we decode the opcode and then use instruction signals to generate desired control signals

# Main Control Signal Logic

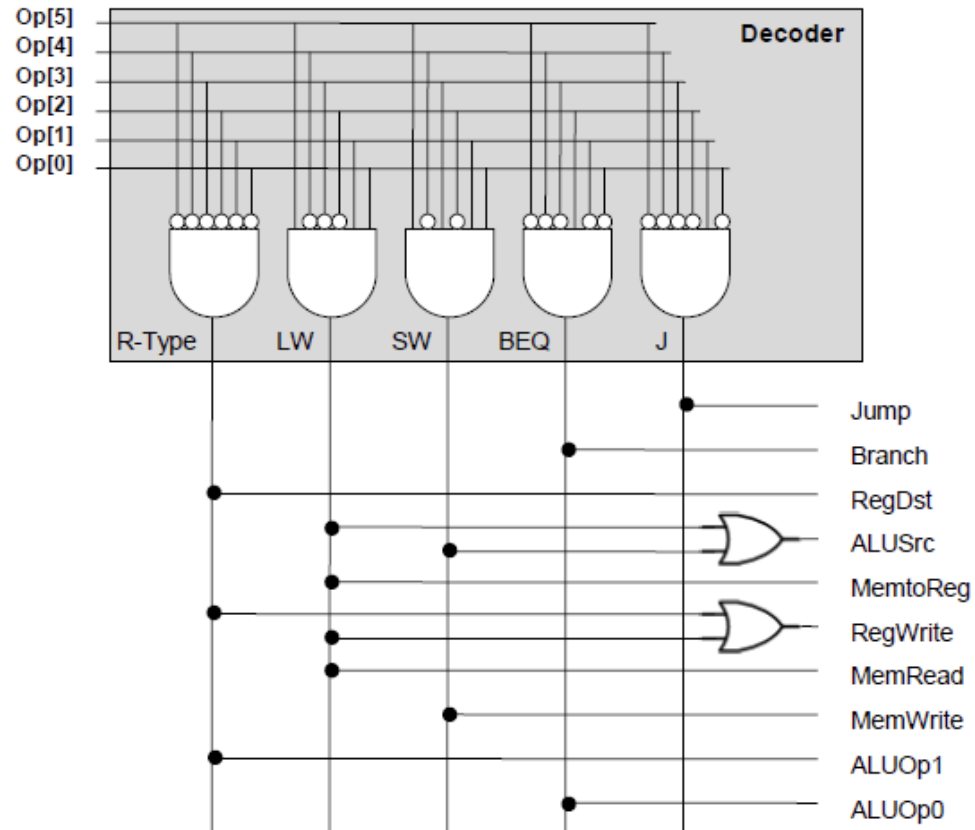


# Main Control Signal Truth Table


R-Type	LW	SW	BEQ	J	Jump	Branch	Reg Dst	ALU Src	Memto-Reg	Reg Write	Mem Read	Mem Write	ALU Op[1]	ALU Op[0]
1	0	0	0	0	0	0	1	0	0	1	0	0	1	0
0	1	0	0	0	0	0	0	1	1	1	1	0	0	0
0	0	1	0	0	0	0	X	1	X	0	0	1	0	0
0	0	0	1	0	0	1	X	0	X	0	0	0	0	1
0	0	0	0	1	1	0	X	X	X	0	0	0	X	X

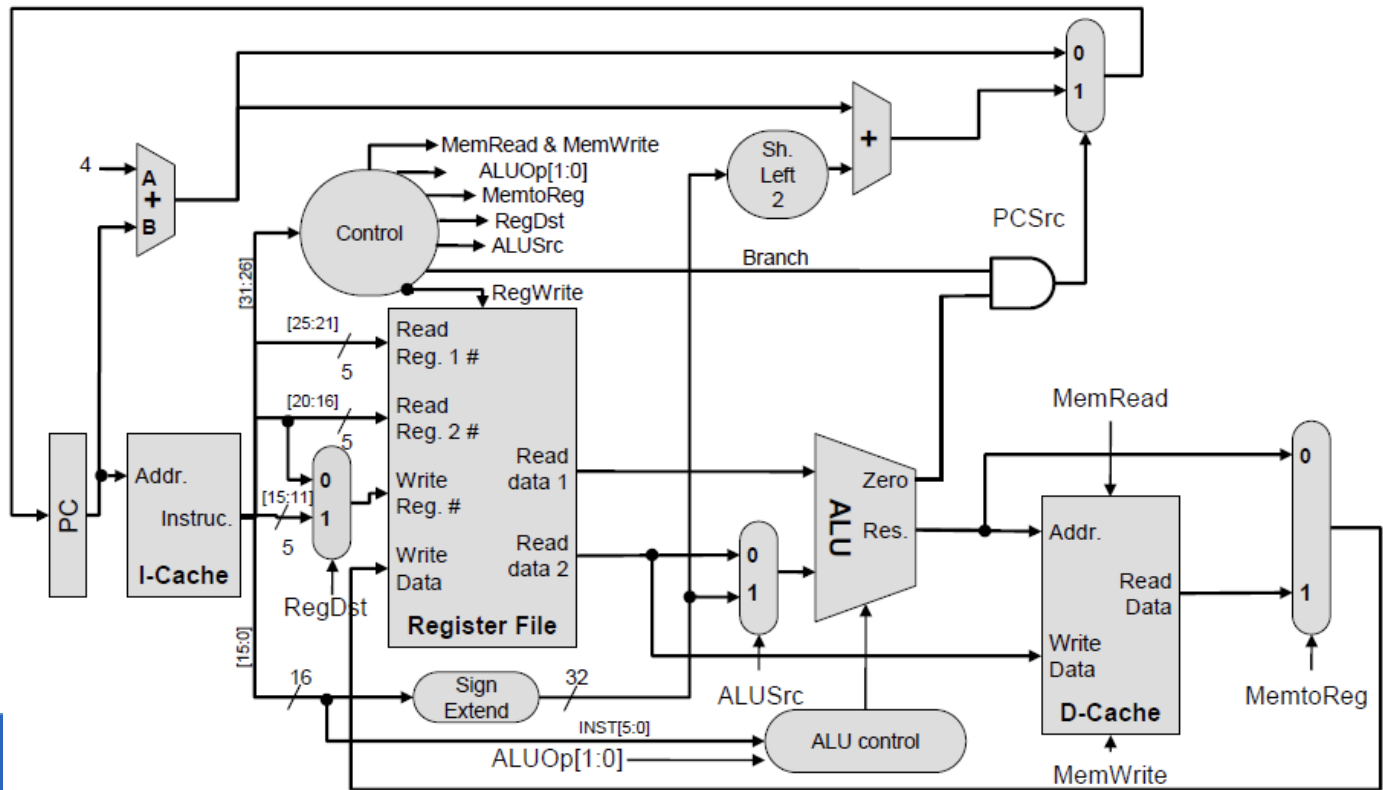

# Review – R-type Instructions

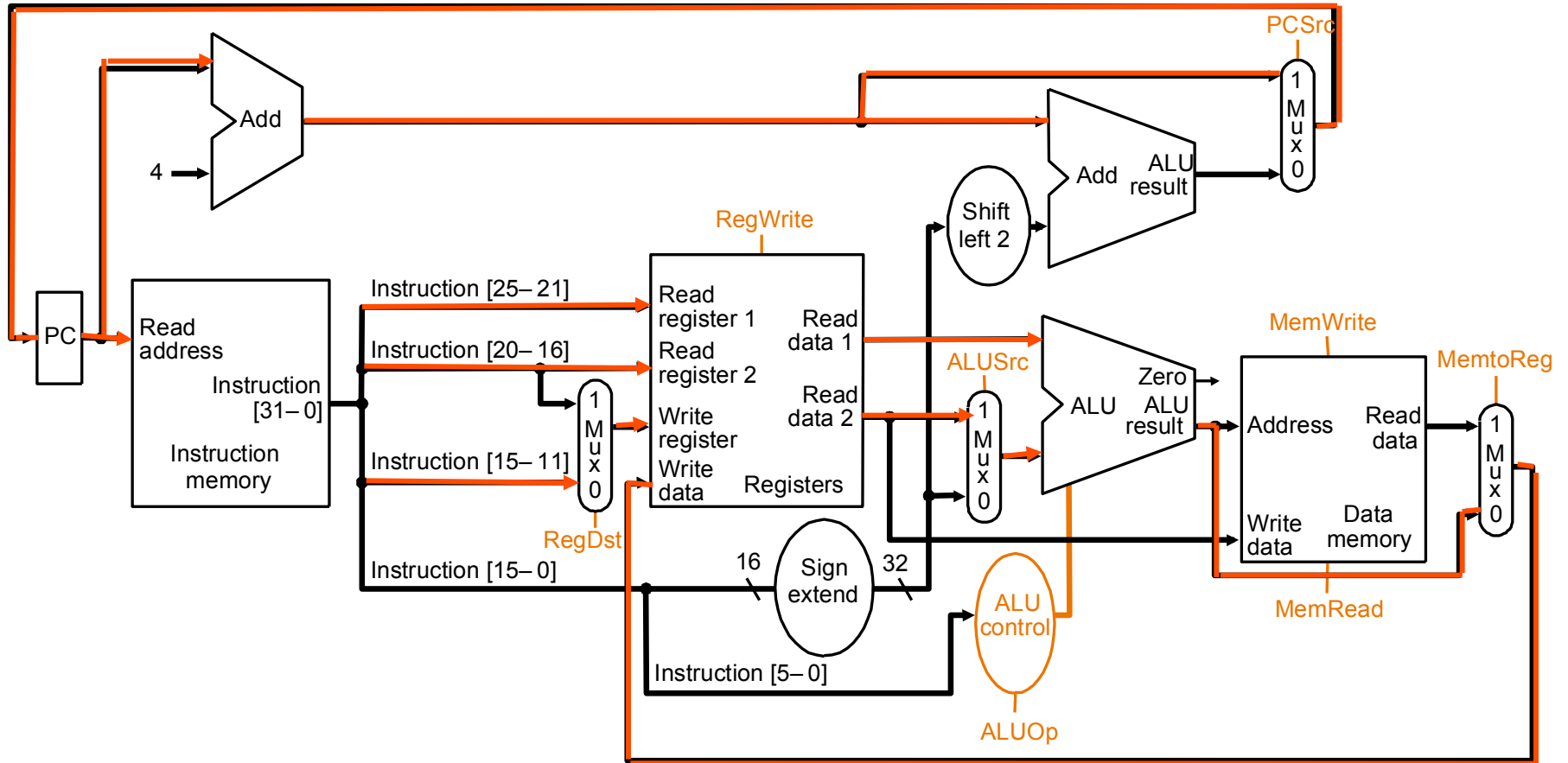


# Review – Lw Instruction

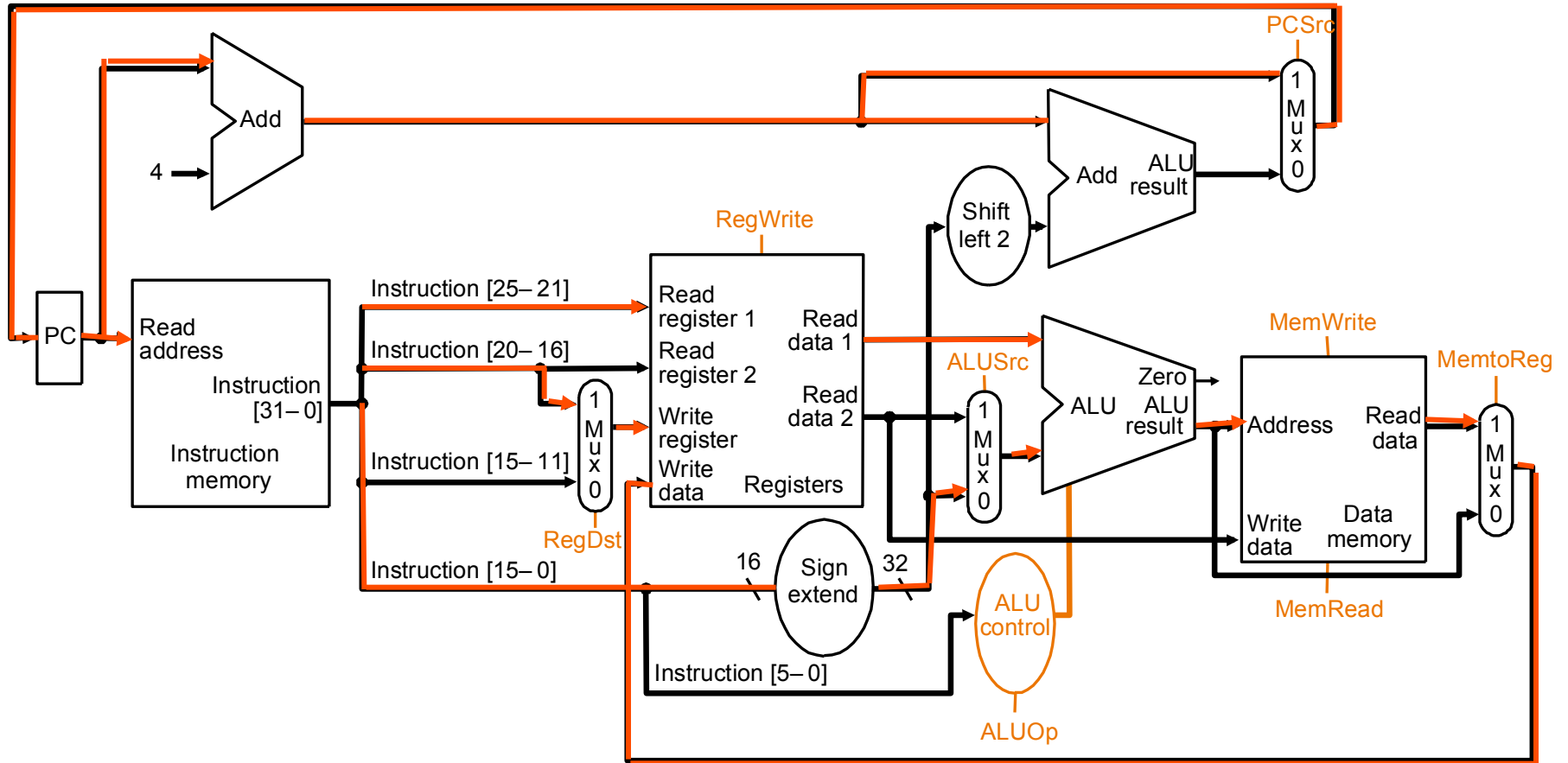




# Review – Branch Instructions

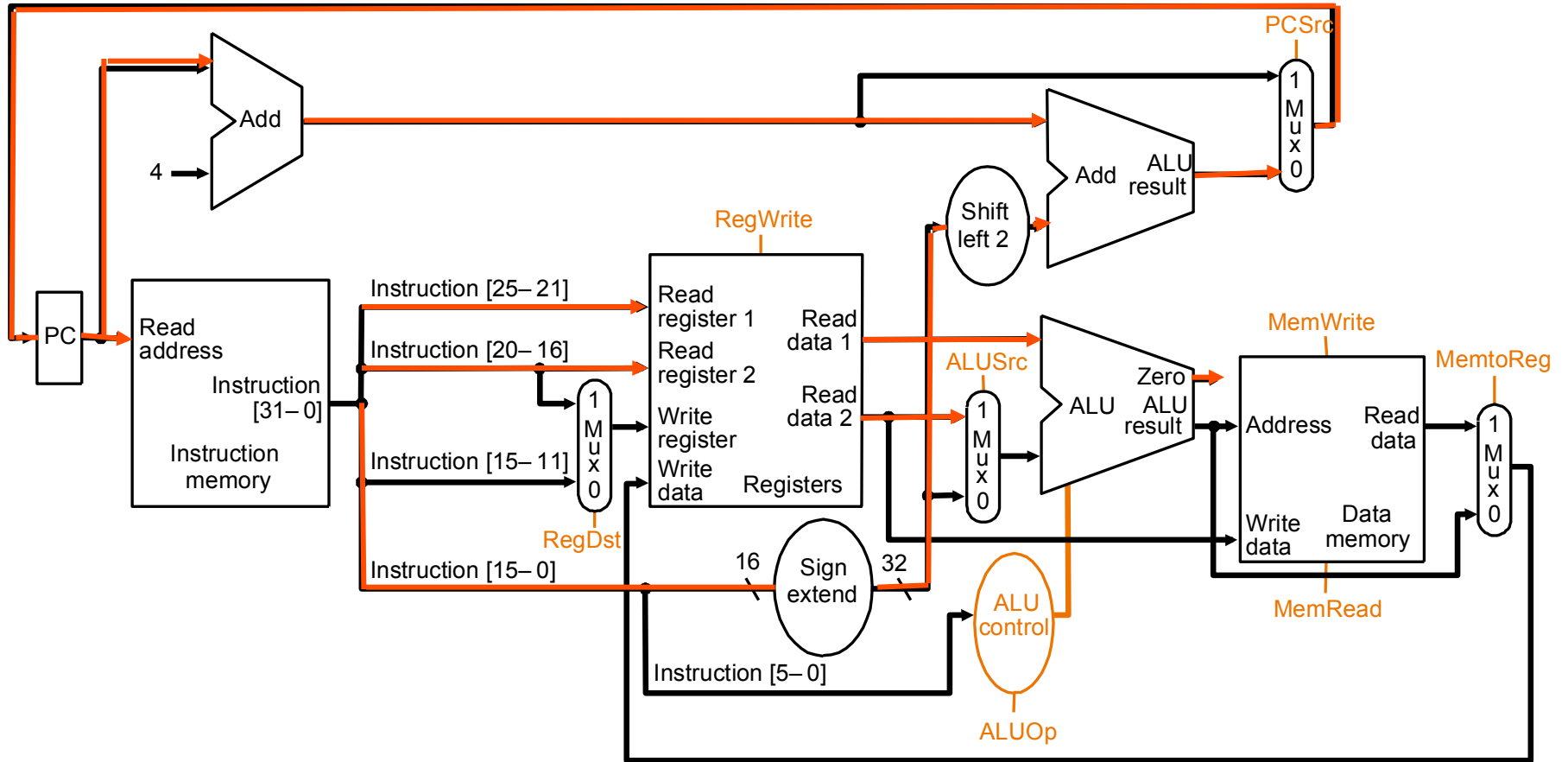

# Jump Instruction

- JAL (Jump and Link) for function calls
- How do we add JAL to datapath?
  - 1. Place  $PC+4$  (return address) into  $\$ra$
  - 2. Extend RegDst mux to include 31 ( $\$ra$ )
  - 3. Extend MemtoReg mux at write data input to have  $PC+4$  as input

# Jump Instruction Implementation

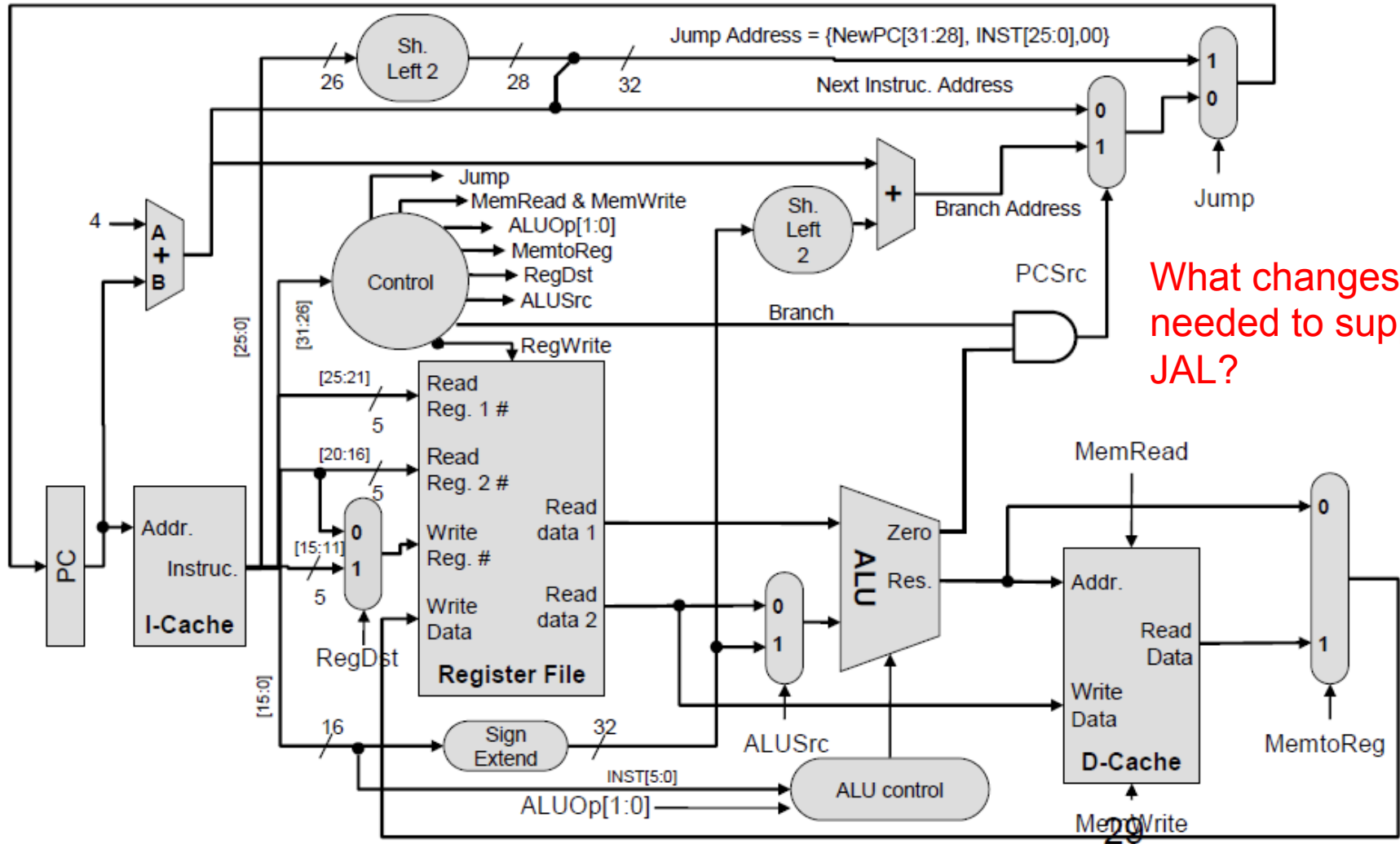

# Acknowledgements



- › Slide sources from:
  - › UCR CS161
    - › Walid Najjar
    - › Laxmi Bhuyan
  - › USC EE457
    - › Mark Redekopp
    - › Gandhi Puvvada