



# Contents

---

Preface iii

Contents ix

## ▶ CHAPTER 1

Introduction 1

- 1.1 Digital Systems in the World Around Us 1
- 1.2 The World of Digital Systems 4
- 1.3 Implementing Digital Systems: Programming Microprocessors versus Designing Digital Circuits 17
- 1.4 About this Book 23
- 1.5 Exercises 24

## ▶ CHAPTER 2

Combinational Logic Design 30

- 2.1 Introduction 30
- 2.2 Switches 30
- 2.3 The CMOS Transistor 35
- 2.4 Boolean Logic Gates—Building Blocks for Digital Circuits 38
- 2.5 Boolean Algebra 47
- 2.6 Representations of Boolean Functions 55
- 2.7 Combinational Logic Design Process 67
- 2.8 More Gates 73
- 2.9 Decoders and Muxes 77
- 2.10 Additional Considerations 83
- 2.11 Combinational Logic Optimizations and Tradeoffs (See Section 6.2) 86
- 2.12 Combinational Logic Description using Hardware Description Languages (See Section 9.2) 86
- 2.13 Chapter Summary 86
- 2.14 Exercises 87

## ▶ CHAPTER 3

Sequential Logic Design—Controllers 95

- 3.1 Introduction 95
- 3.2 Storing One Bit—Flip-Flops 96

3.3 Finite-State Machines (FSMs) and Controllers 111

3.4 Controller Design 120

3.5 More on Flip-Flops and Controllers 130

3.6 Sequential Logic Optimizations and Tradeoffs (See Section 6.3) 137

3.7 Sequential Logic Description using Hardware Description Languages (See Section 9.3) 137

3.8 Product Profile—Pacemaker 137

3.9 Chapter Summary 140

3.10 Exercises 140

## ▶ CHAPTER 4

Datapath Components 150

- 4.1 Introduction 150
- 4.2 Registers 151
- 4.3 Adders 165
- 4.4 Shifters 173
- 4.5 Comparators 177
- 4.6 Counters 181
- 4.7 Multiplier—Array Style 189
- 4.8 Subtractors 190
- 4.9 Arithmetic-Logic Units—ALUs 201
- 4.10 Register Files 204
- 4.11 Datapath Component Tradeoffs (See Section 6.4) 209
- 4.12 Datapath Component Description using Hardware Description Languages (See Section 9.4) 209
- 4.13 Chapter Summary 216
- 4.14 Exercises 217

## ▶ CHAPTER 5

Register-Transfer Level (RTL) Design 225

- 5.1 Introduction 225
- 5.2 RTL Design Method 226
- 5.3 RTL Design Examples and Issues 238
- 5.4 Determining Clock Frequency 251

- 5.5 Behavioral-Level Design: C to Gates (Optional) **254**
- 5.6 Memory Components **258**
- 5.7 Queues (FIFOs) **271**
- 5.8 Hierarchy—A Key Design Concept **275**
- 5.9 RTL Design Optimizations and Tradeoffs (See Section 6.5) **278**
- 5.10 RTL Design using Hardware Description Languages (See Section 9.5) **279**
- 5.11 Product Profile: Cell Phone **279**
- 5.12 Chapter Summary **285**
- 5.13 Exercises **285**

► **CHAPTER 6**

- Optimizations and Tradeoffs **294**
- 6.1 Introduction **294**
- 6.2 Combinational Logic Optimizations and Tradeoffs **296**
- 6.3 Sequential Logic Optimizations and Tradeoffs **317**
- 6.4 Datapath Component Tradeoffs **333**
- 6.5 RTL Design Optimizations and Tradeoffs **345**
- 6.6 More on Optimizations and Tradeoffs **354**
- 6.7 Product Profile: Digital Video Player/Recorder **361**
- 6.8 Chapter Summary **370**
- 6.9 Exercises **370**

► **CHAPTER 7**

- Physical Implementation **379**
- 7.1 Introduction **379**
- 7.2 Manufactured IC Technologies **379**
- 7.3 Programmable IC Technology—FPGA **388**
- 7.4 Other Technologies **401**
- 7.5 IC Technology Comparisons **409**
- 7.6 Product Profile: Giant Video Display **412**
- 7.7 Chapter Summary **416**
- 7.8 Exercises **417**

► **CHAPTER 8**

- Programmable Processors **421**
- 8.1 Introduction **421**
- 8.2 Basic Architecture **422**
- 8.3 A Three-Instruction Programmable Processor **428**

- 8.4 A Six-Instruction Programmable Processor **434**
- 8.5 Example Assembly and Machine Programs **438**
- 8.6 Further Extensions to the Programmable Processor **439**
- 8.7 Chapter Summary **441**
- 8.8 Exercises **442**

► **CHAPTER 9**

- Hardware Description Languages **445**
- 9.1 Introduction **445**
- 9.2 Combinational Logic Description Using Hardware Description Languages **447**
- 9.3 Sequential Logic Description Using Hardware Description Languages **459**
- 9.4 Datapath Component Description Using Hardware Description Languages **467**
- 9.5 RTL Design Using Hardware Description Languages **475**
- 9.6 Chapter Summary **492**
- 9.7 Exercises **492**

► **APPENDIX A**

- Boolean Algebras **496**
- A.1 Boolean Algebra **496**
- A.2 Switching Algebra **497**
- A.3 Important Theorems in Boolean Algebra **498**
- A.4 Other Examples of Boolean Algebras **504**
- A.5 Further Readings **504**

► **APPENDIX B**

- Additional Topics in Binary Number Systems **505**
- B.1 Introduction **505**
- B.2 Real Number Representation **505**
- B.3 Fixed Point Arithmetic **508**
- B.4 Floating Point Representation **509**
- B.5 Exercises **514**

► **APPENDIX C**

- Extended RTL Design Example **515**
- C.1 Introduction **515**
- C.2 Designing the Soda Dispenser Controller **516**
- C.3 Understanding the Behavior of the Soda Dispenser Controller and Datapath **519**
- Index **526**