
CSE 161 – Design and Architecture of Computer Systems

Chapter Six

Simple Questions

- ❑ How many cycles will it take to execute this code?

```
lw $t2, 0($t3)
lw $t3, 4($t3)
beq $t2, $t3, Label ← #assume not
add $t5, $t2, $t3
sw $t5, 8($t3)
```



Label: ...

- ❑ What is going on during the 8th cycle of execution?
- ❑ In what cycle does the actual addition of \$t2 and \$t3 takes place?



Pipelining

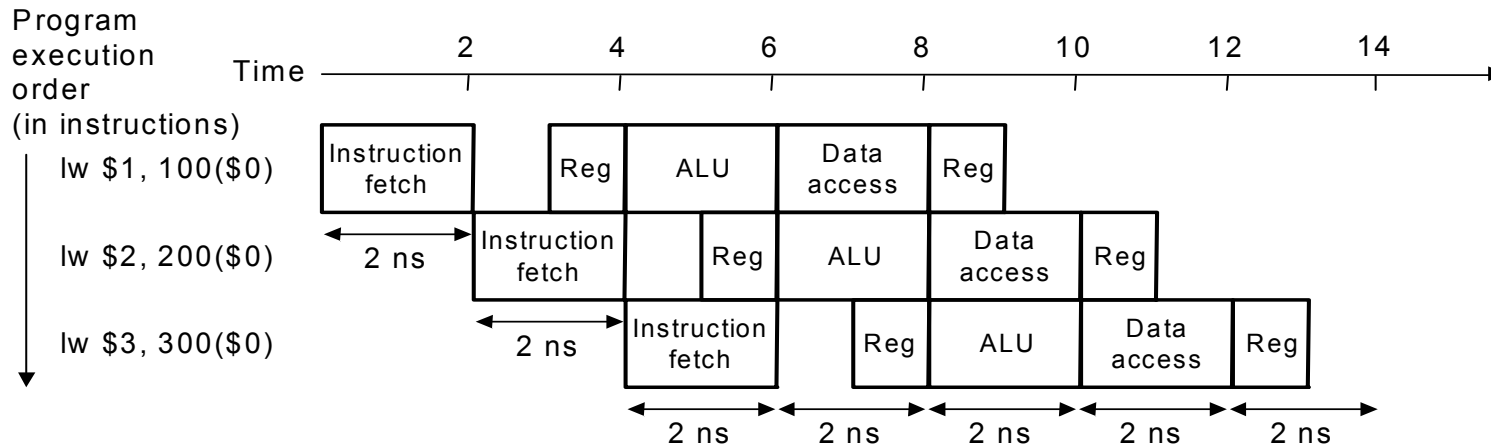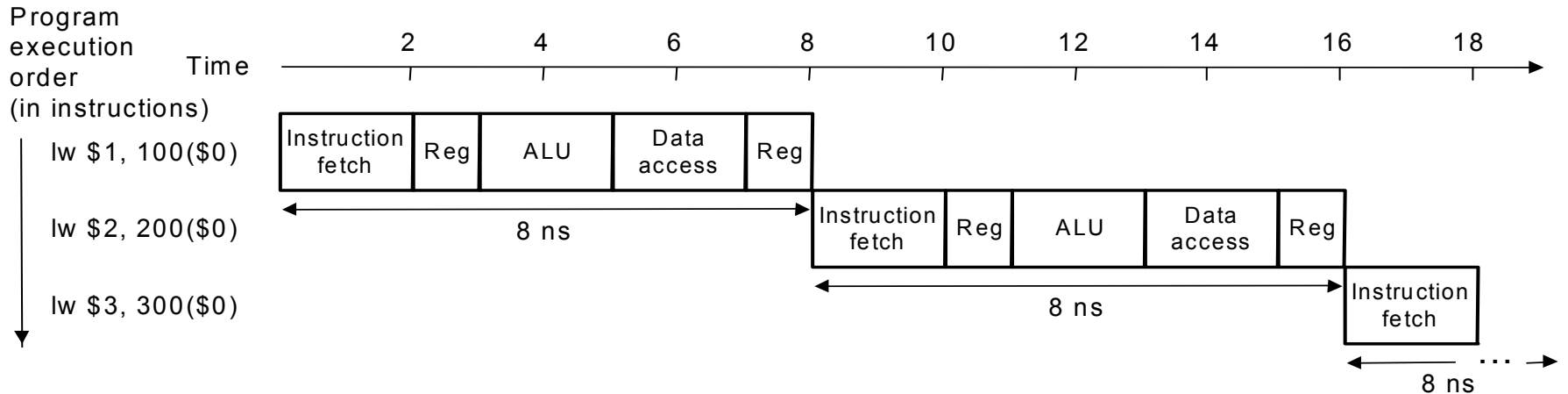- Improve performance by increasing instruction throughput



Ideal speedup is number of stages in the pipeline. Do we achieve this?

Pipelining


- ❑ **What makes it easy**
 - all instructions are the same length
 - just a few instruction formats
 - memory operands appear only in loads and stores

- ❑ **What makes it hard?**
 - structural hazards: suppose we had only one memory
 - control hazards: need to worry about branch instructions
 - data hazards: an instruction depends on a previous instruction

- ❑ **We'll build a simple pipeline and look at these issues**


- ❑ **We'll talk about modern processors and what really makes it hard:**
 - exception handling
 - trying to improve performance with out-of-order execution, etc.

Basic Idea

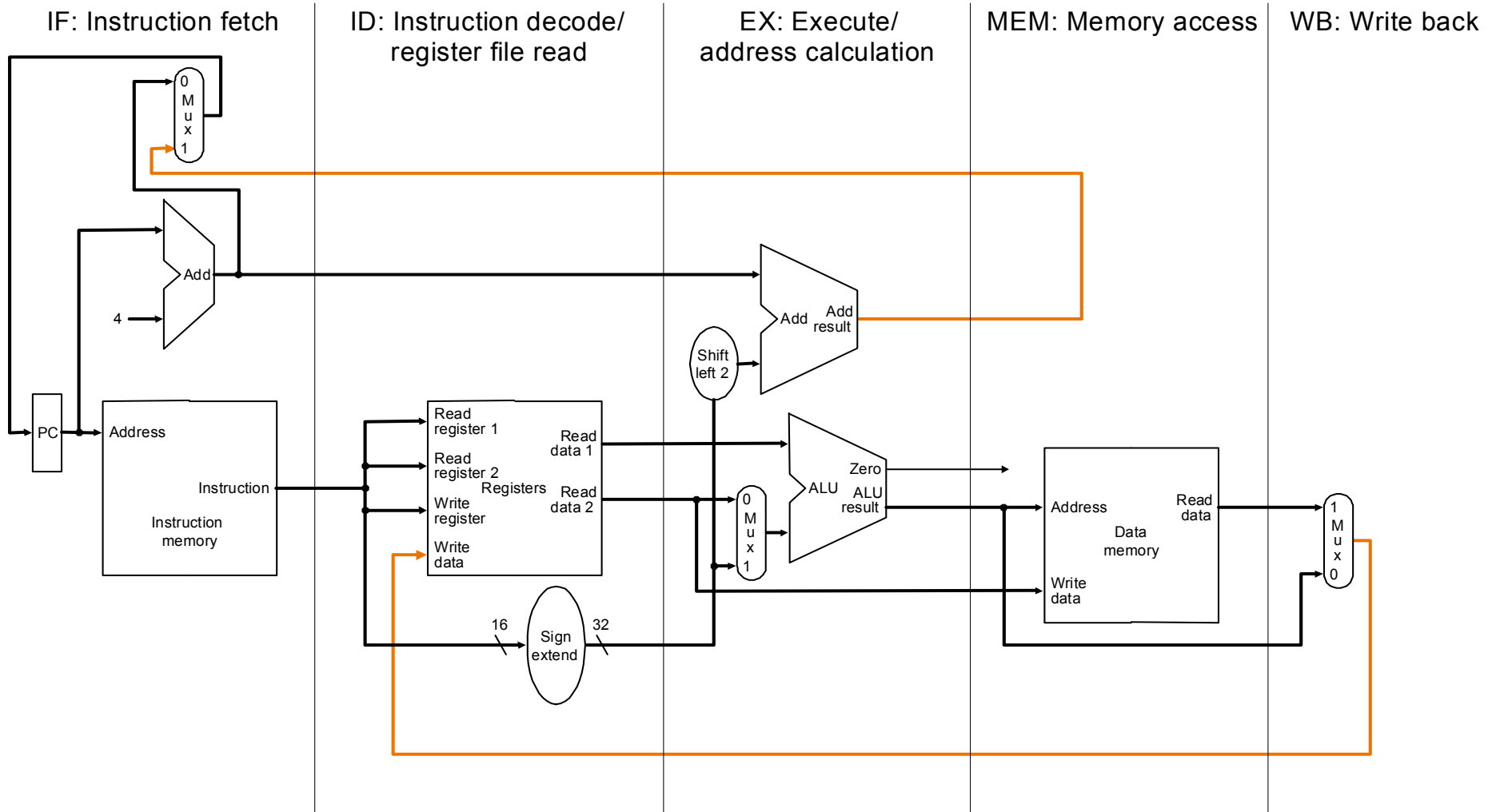


□ *What do we need to add to actually split the datapath into stages?*


Pipelined Datapath

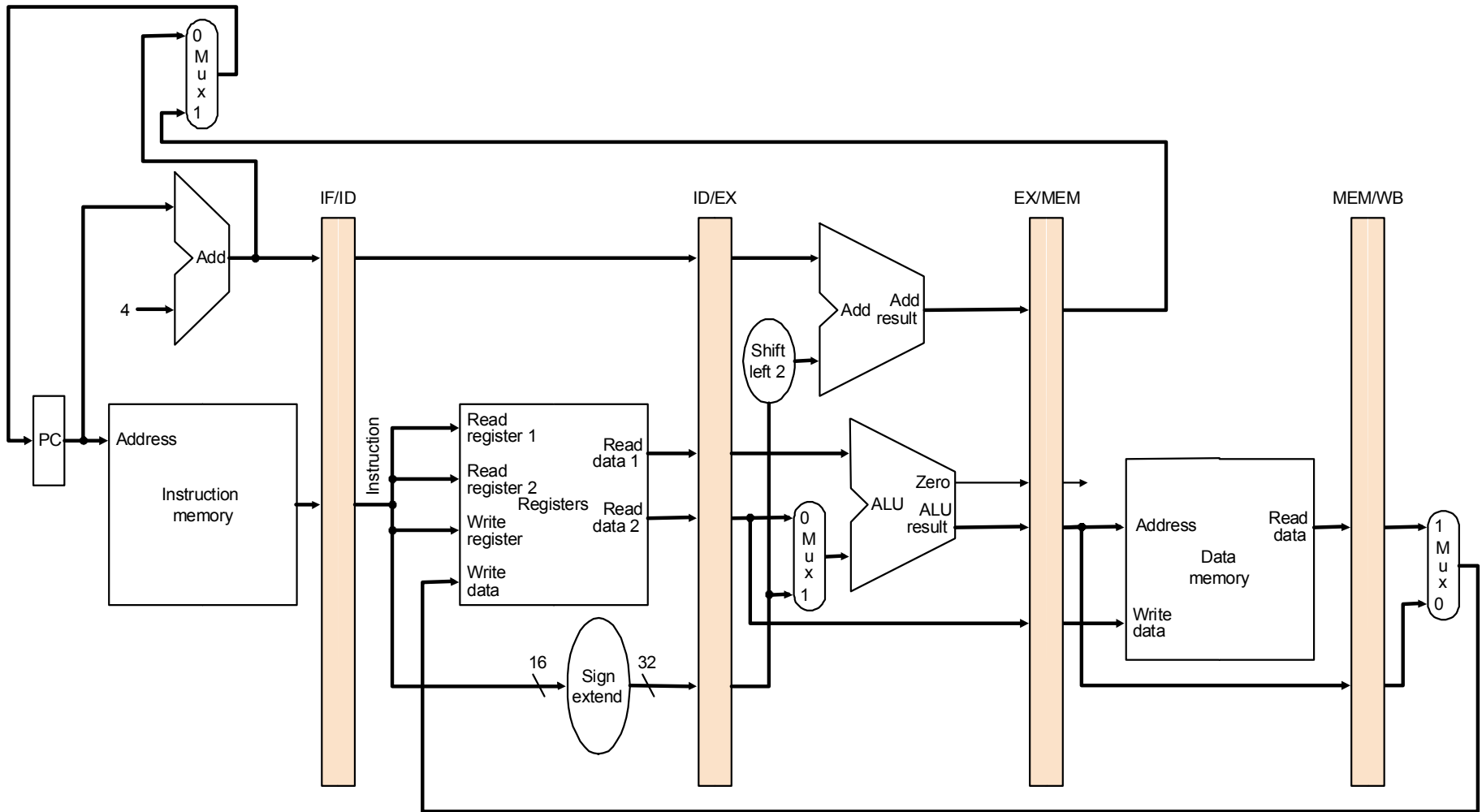

Corrected Datapath

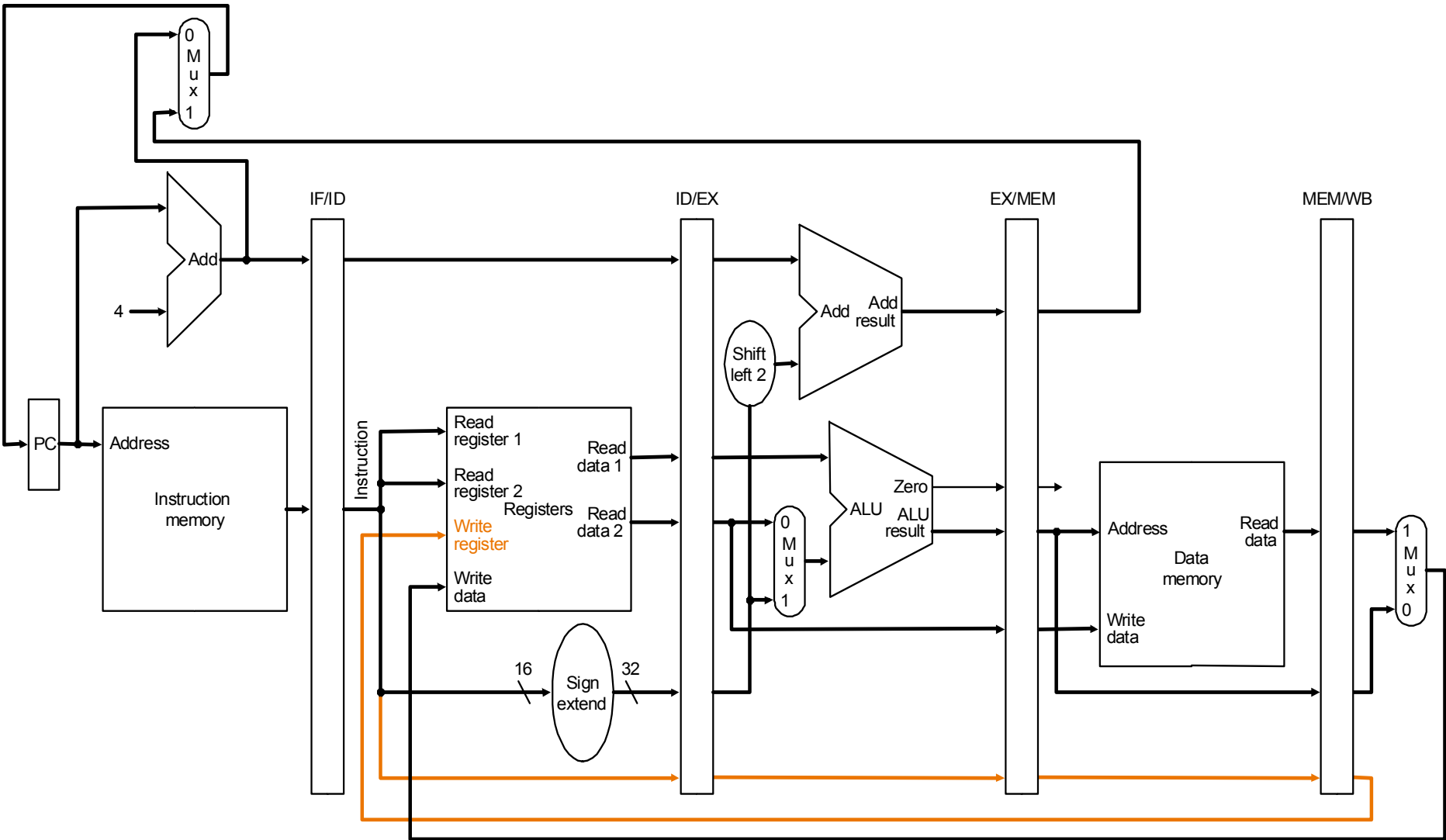


Graphically Representing Pipelines

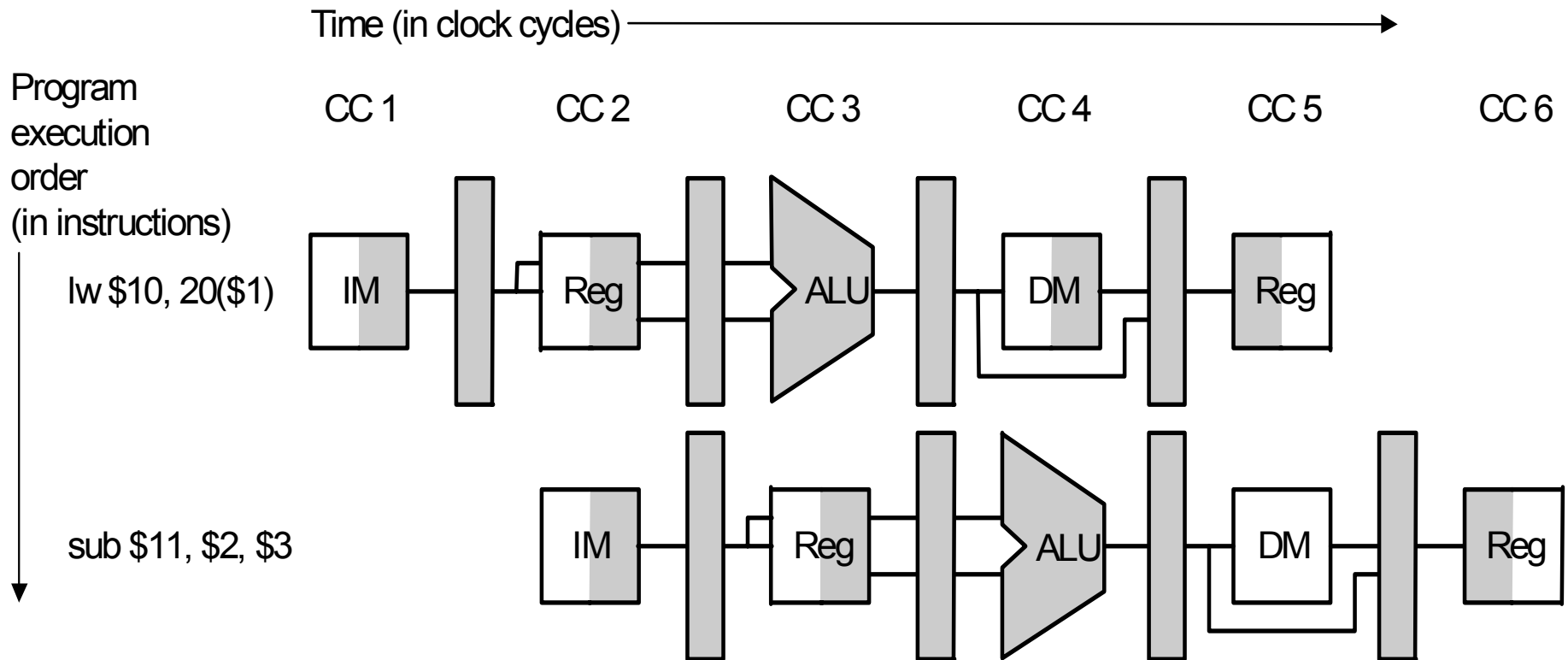

□ Can help with answering questions like:

- how many cycles does it take to execute this code?
- what is the ALU doing during cycle 4?
- use this representation to help understand datapaths

Pipeline Control

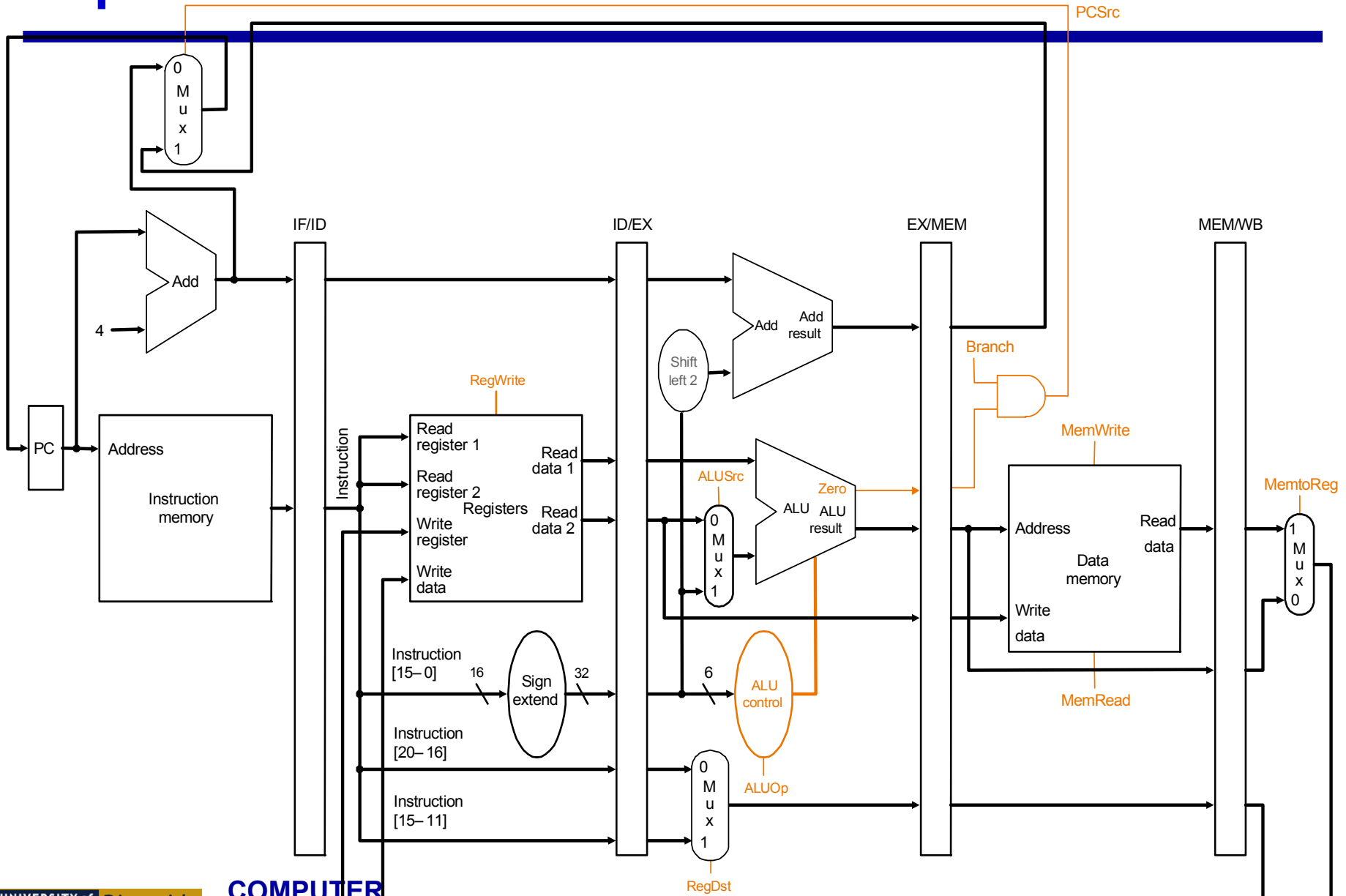

Pipeline control


- ❑ **We have 5 stages. What needs to be controlled in each stage?**
 - **Instruction Fetch and PC Increment**
 - **Instruction Decode / Register Fetch**
 - **Execution**
 - **Memory Stage**
 - **Write Back**

- ❑ **How would control be handled in an automobile plant?**
 - **a fancy control center telling everyone what to do?**
 - **should we use a finite state machine?**

Pipeline Control

- Pass control signals along just like the data

Instruction	Execution/Address Calculation stage control lines				Memory access stage control lines			stage control lines	
	Reg Dst	ALU Op1	ALU Op0	ALU Src	Branch	Mem Read	Mem Write	Reg write	Mem to Reg
R-format	1	1	0	0	0	0	0	1	0
lw	0	0	0	1	0	1	0	1	1
sw	X	0	0	1	0	0	1	0	X
beq	X	0	1	0	1	0	0	0	X

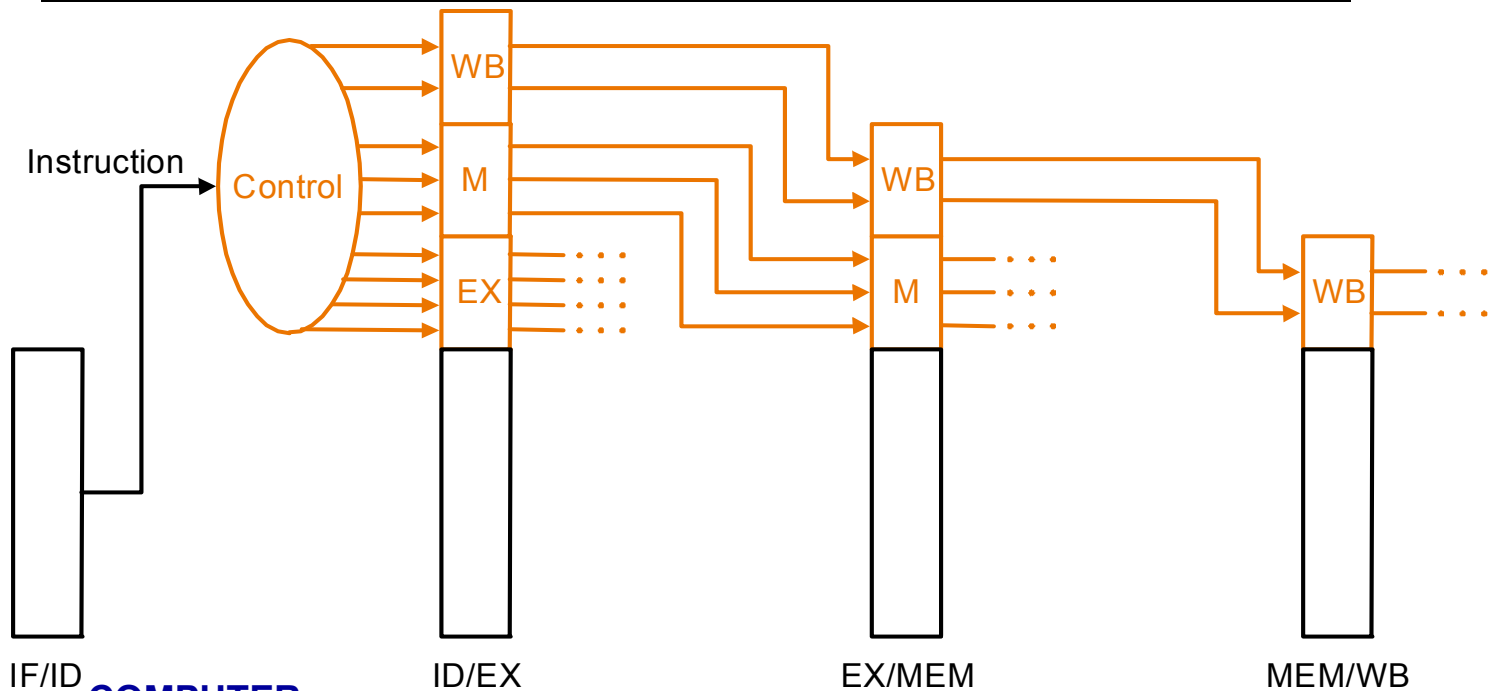

IF/ID

ID/EX

EX/MEM

MEM/WB

Datapath with Control

